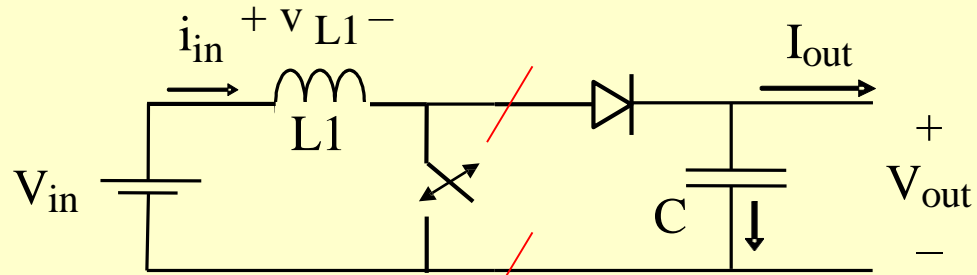




SEPIC CONVERTER

Prepared by
V.Pandiyan M.E.,


Boost converter



SEPIC converter

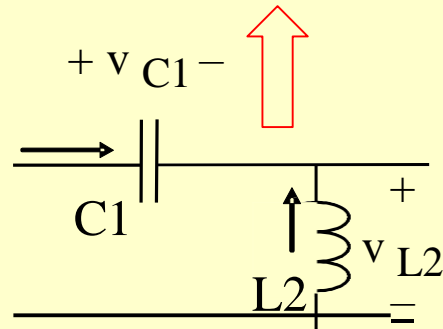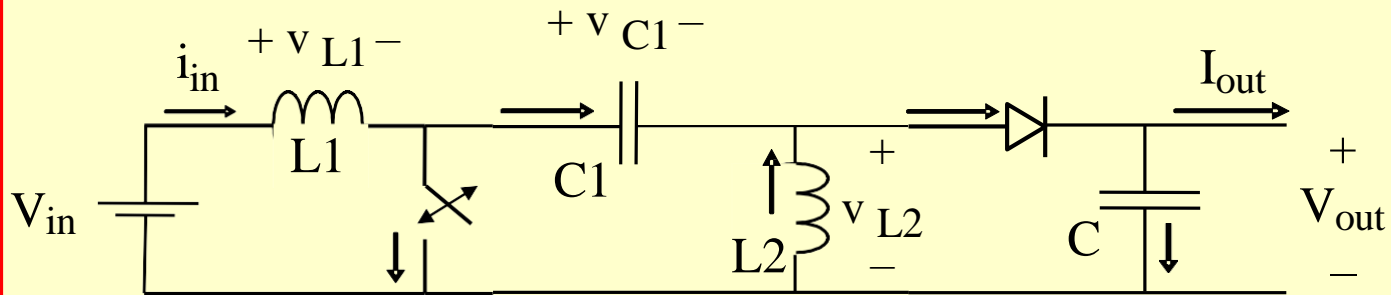

SEPIC converter

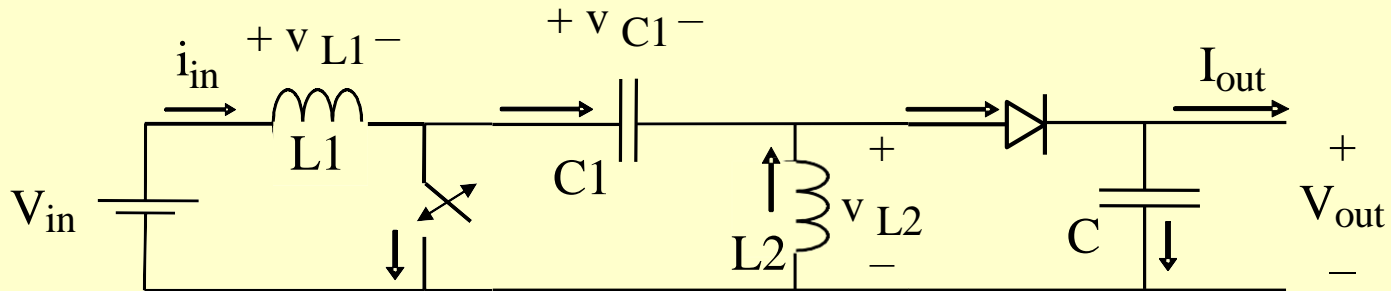


SEPIC = single ended primary inductor converter

This circuit is more unforgiving than the boost converter, because the MOSFET and diode voltages and currents are higher


- **Before applying power, make sure that your D is at the minimum, and that a load is solidly connected**
- **Limit your output voltage to 90V**

KVL and KCL in the average sense

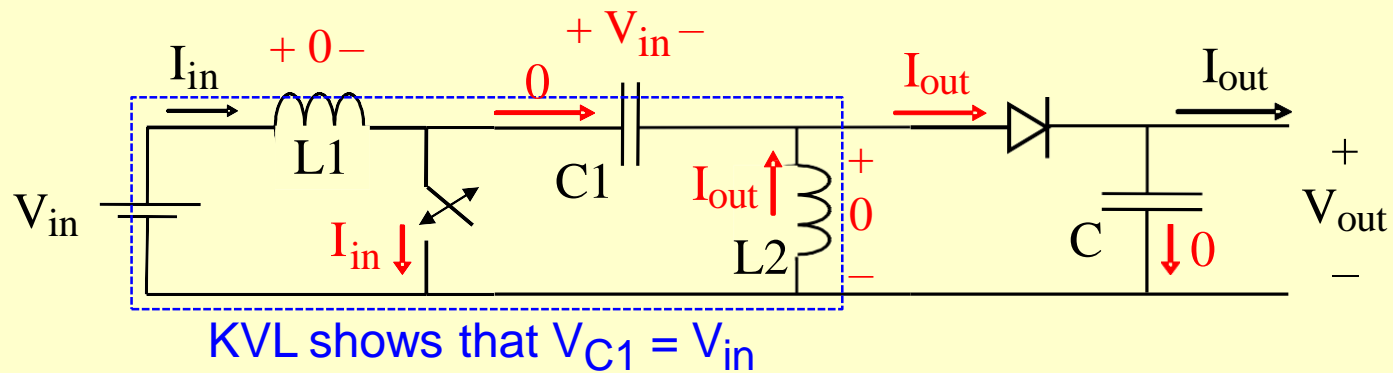


Interestingly, no average current passes from the source side, through $C1$, to the load side, and yet this is a “DC - DC” converter

Switch closed

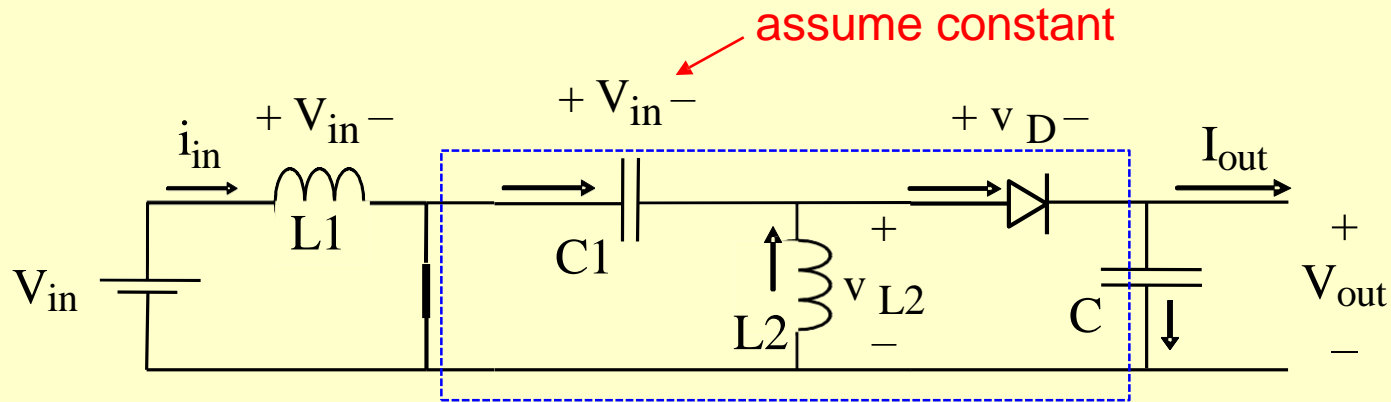


KVL shows that $v_D = -(V_{in} + V_{out})$,
so the diode is open

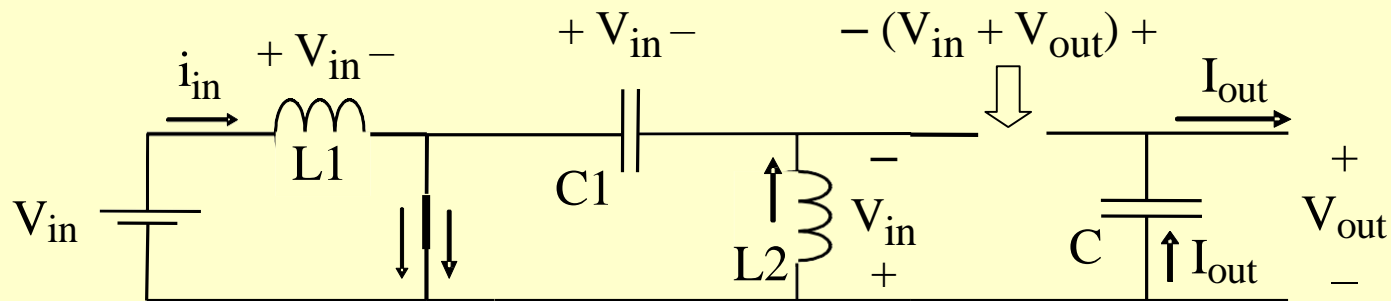Thus, C is providing the load power when the switch is closed



i_{L1} and i_{L2} are ramping up (charging). C1 is charging L2
(so C1 is discharging). C is also discharging.

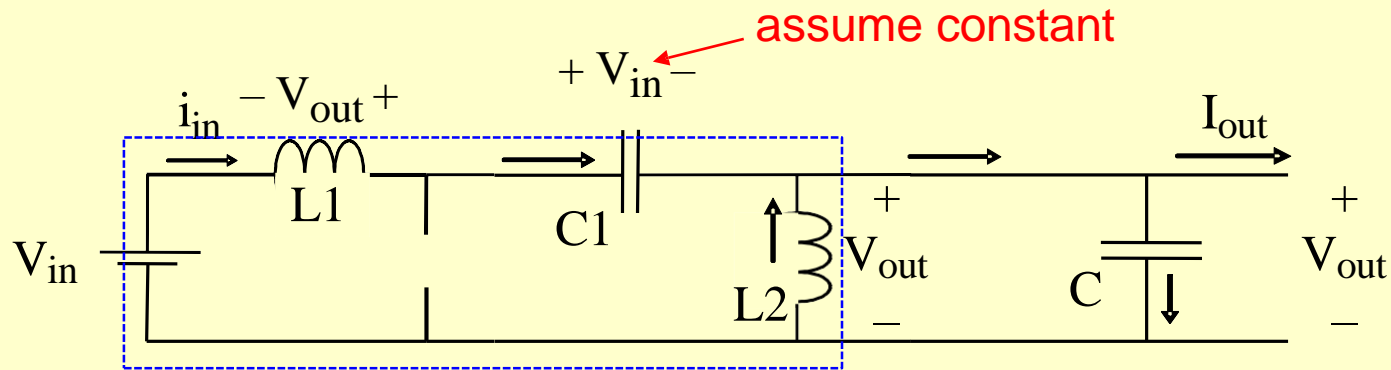Switch open (assume the diode is conducting because, otherwise, the circuit cannot work)



C1 and C are charging. L1 and L2 are discharging.

KVL shows that $V_{L1} = -V_{out}$

The input/output equation comes from recognizing that the average voltage across L1 is zero


$$V_{L1avg} = D \cdot V_{in} + (1-D) \cdot (-V_{out}) = 0$$

$$V_{out} \cdot (1-D) = D \cdot V_{in}$$

$$V_{out} = \frac{DV_{in}}{1-D}$$

Voltage can be stepped-up or stepped-down

The buck-boost converter

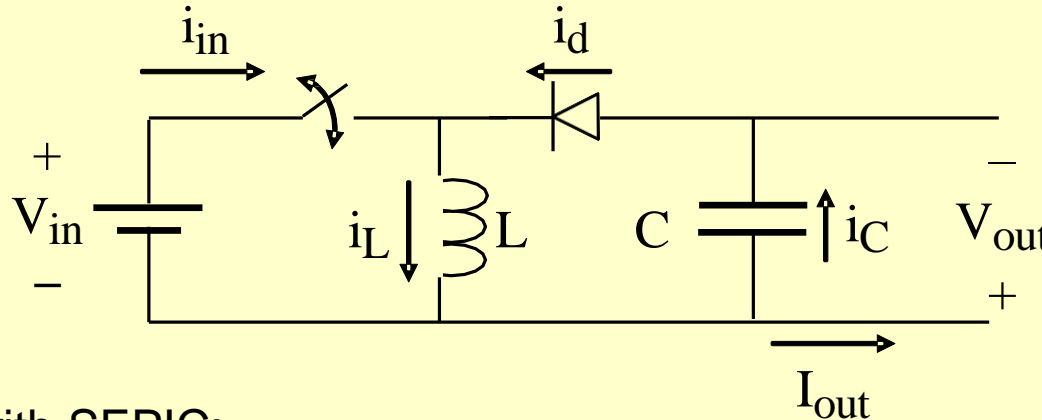

Inverse polarity
with respect to
input

Compared with SEPIC:

- + Fewer energy storage components
- + Capacitor does not carry load current
- + In both converters isolation can be easily implemented
- Polarity is reversed

$$V_{out} = \frac{DV_{in}}{1-D}$$

Voltage can be stepped-up or stepped-down

Inductor L1 current rating



During the “on” state, L1 operates under the same conditions as the boost converter L, so the results are the same

$$I_{L1rms} = \frac{2}{\sqrt{3}} I_{in}$$

Use max

Inductor L2 current rating

Average values


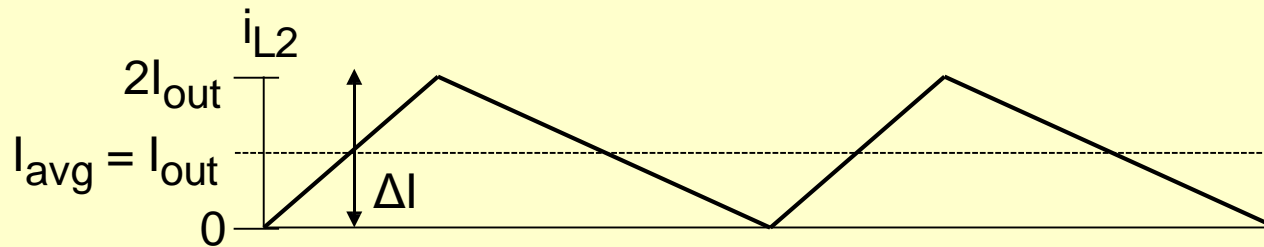
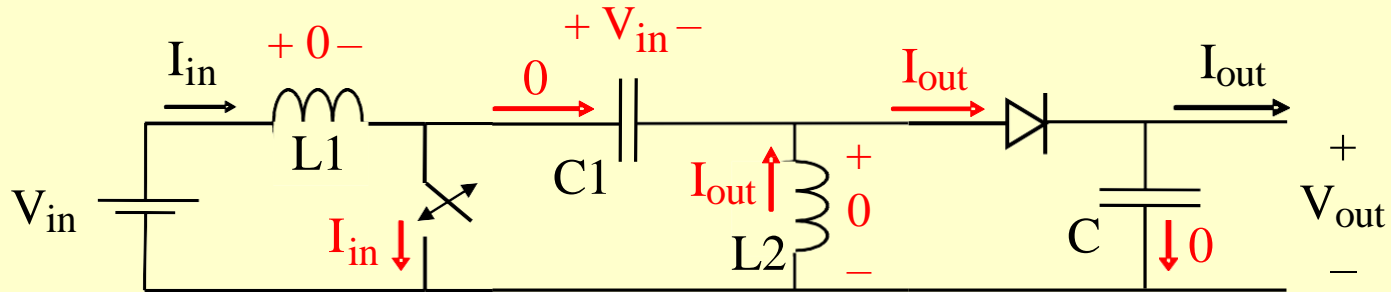


$$I_{L2rms}^2 = I_{out}^2 + \frac{1}{12} (2\Delta I_{out})^2 = \frac{4}{3} I_{out}^2$$

$$I_{L2rms} = \frac{2}{\sqrt{3}} I_{out}$$

Use max

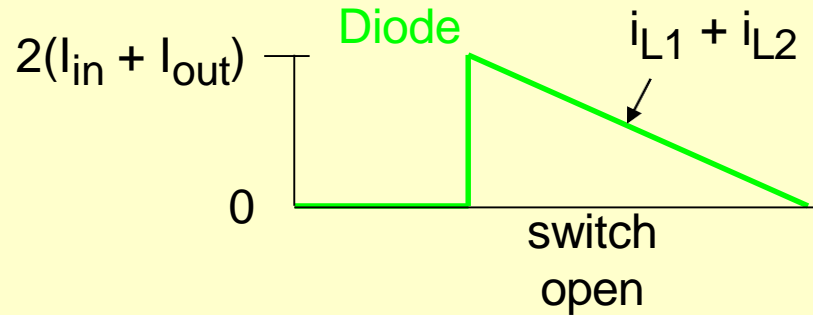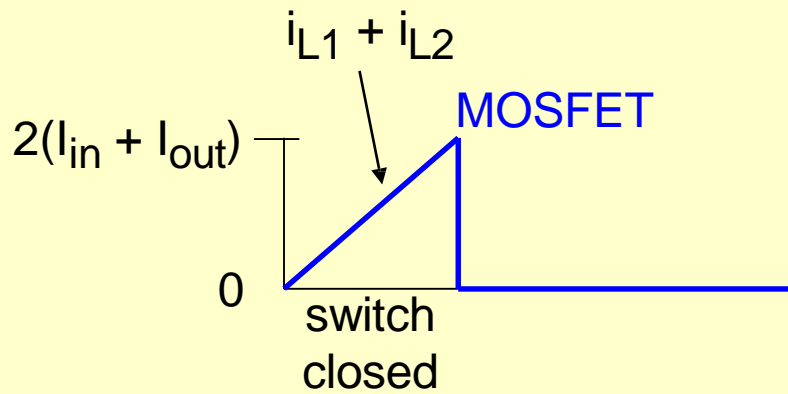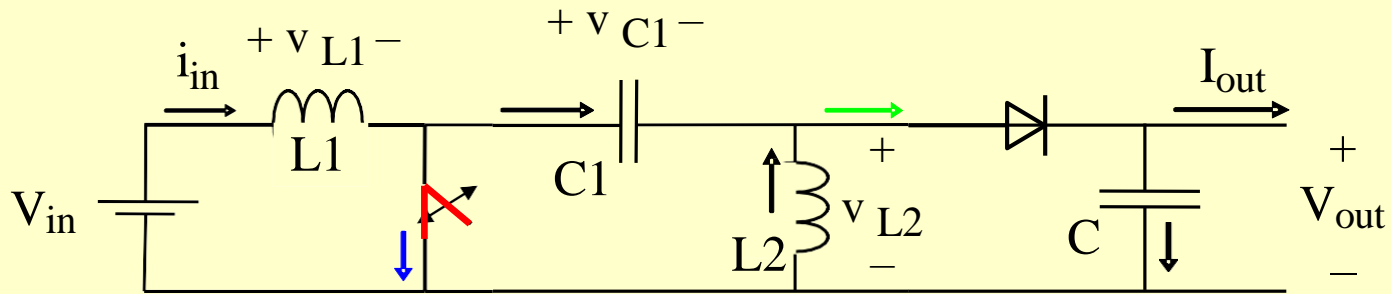MOSFET and diode currents and current ratings




Take worst case D for each

Use max

$$I_{rms} = \frac{2}{\sqrt{3}} (I_{in} + I_{out})$$

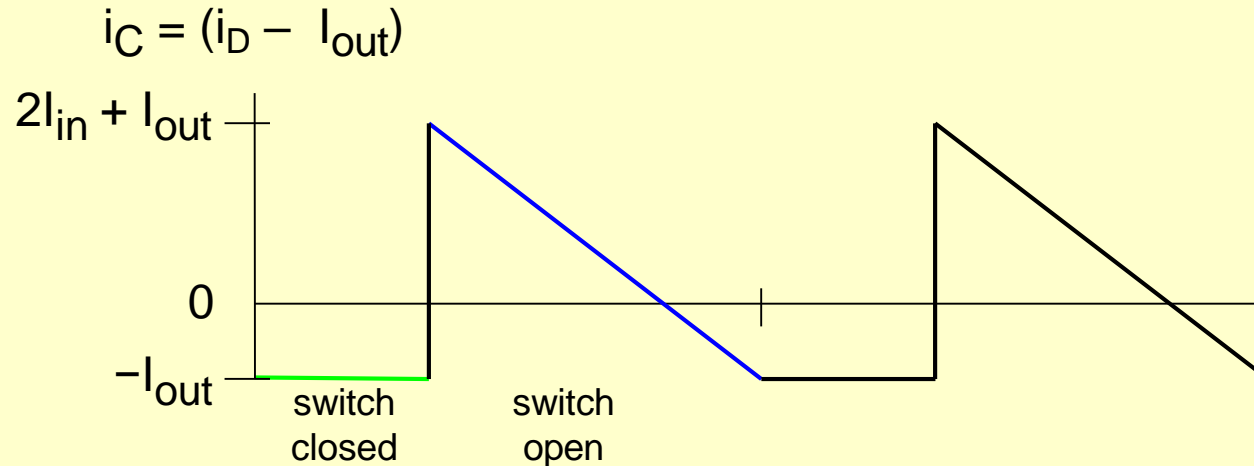Output capacitor C current and current rating





$$I_{in} = \frac{DI_{out}}{1-D}, I_{out} = \frac{(1-D)I_{in}}{D}$$

As $D \rightarrow 1$, $I_{in} \gg I_{out}$, so $I_{Crms} = \frac{2}{\sqrt{3}} I_{in}$

As $D \rightarrow 0$, $I_{in} \ll I_{out}$, so $I_{Crms} = I_{out}$

$$I_{Crms} = \max\left(\frac{2}{\sqrt{3}} I_{in}, I_{out}\right)$$

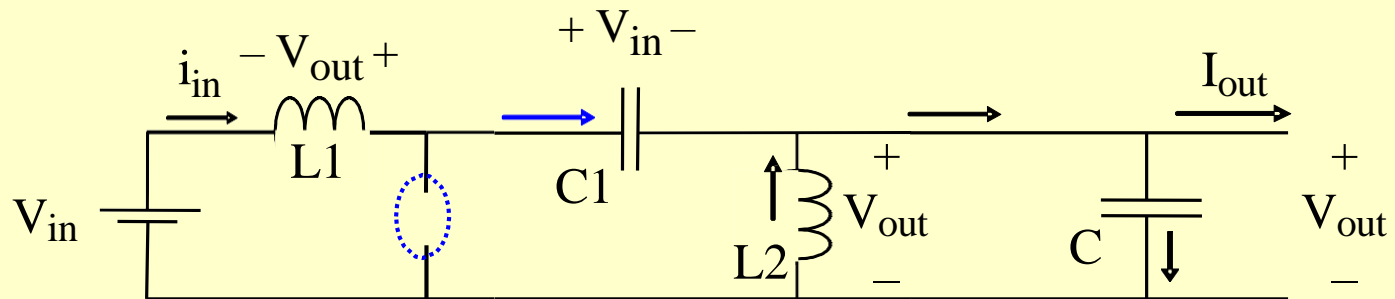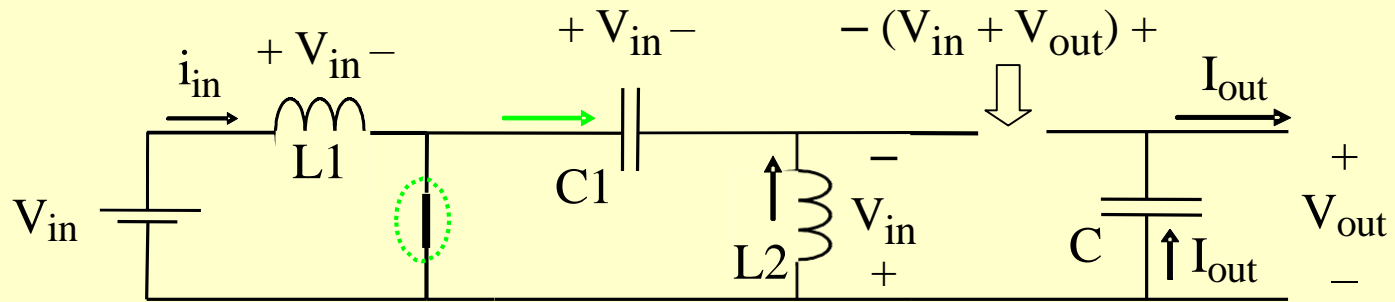
Series capacitor C1 current and current rating



Switch closed, $I_{C1} = -I_{L2}$

Switch open, $I_{C1} = I_{L1}$

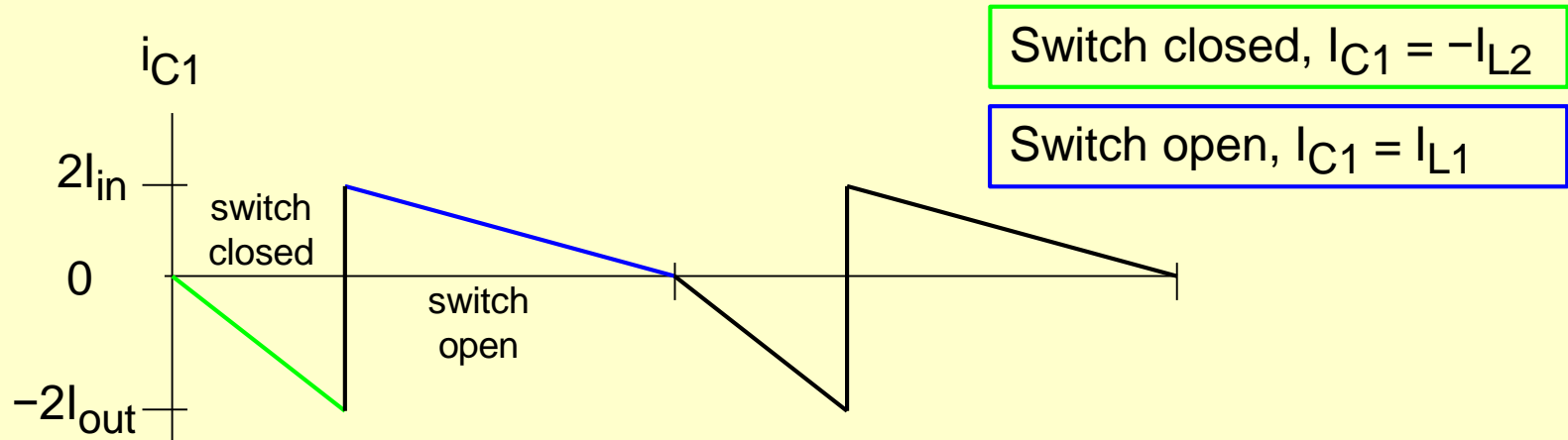Series capacitor C1 current and current rating




As $D \rightarrow 1$, $I_{in} \gg I_{out}$, so $I_{C1rms} = \frac{2}{\sqrt{3}} I_{in}$

As $D \rightarrow 0$, $I_{in} \ll I_{out}$, so $I_{C1rms} = \frac{2}{\sqrt{3}} I_{out}$

$$I_{C1rms} = \max\left(\frac{2}{\sqrt{3}} I_{in}, \frac{2}{\sqrt{3}} I_{out}\right)$$

The high capacitor current rating is a disadvantage of this converter


Worst-case load ripple voltage

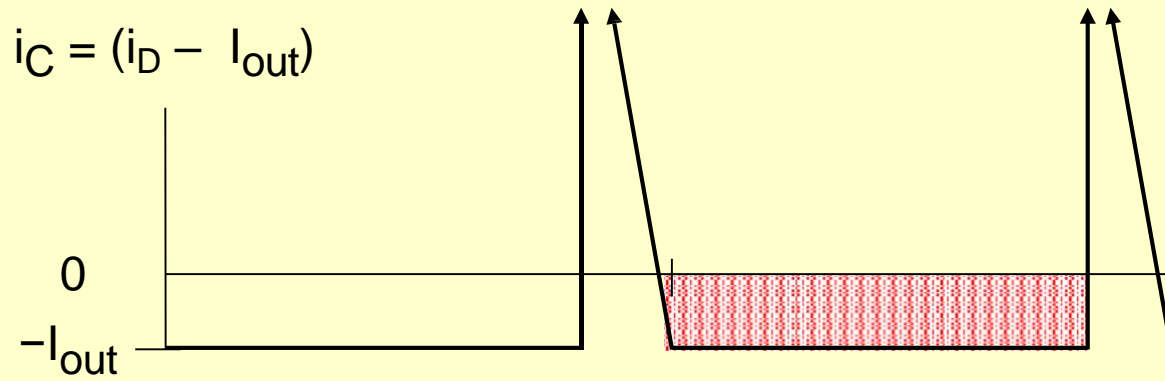

The worst case is where $D \rightarrow 1$, where output capacitor C provides I_{out} for most of the period. Then,

$$\Delta V = \frac{\Delta Q}{C} = \frac{I_{out} \cdot T}{C} = \frac{I_{out}}{Cf}$$

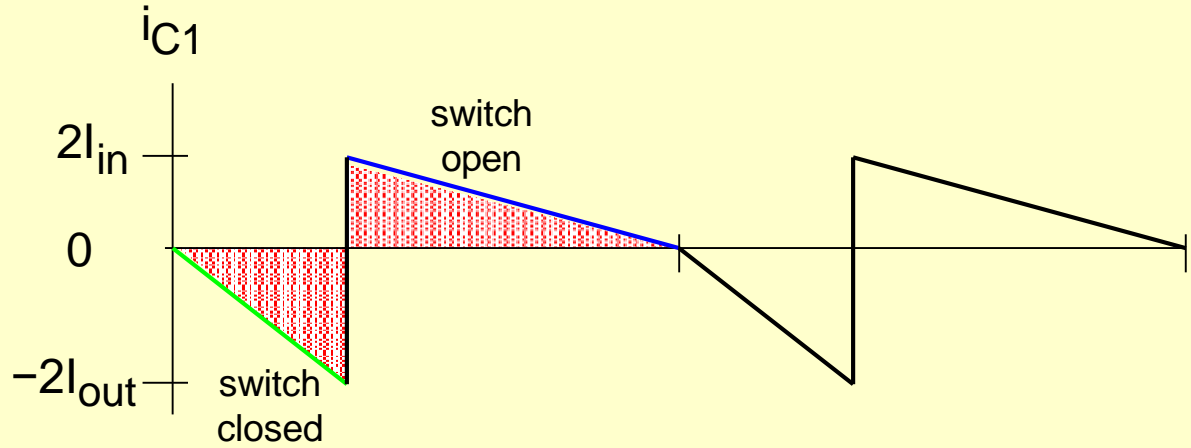Worst case ripple voltage on series capacitor C1




$$\Delta V = \frac{\Delta Q}{C1} = \frac{I_{out} \cdot DT}{C1} = \frac{I_{in} \cdot (1-D)T}{C1}$$


Then, considering the worst case (i.e., D = 1)

$$\Delta V = \frac{I_{out}}{C1 \cdot f}$$

Voltage ratings

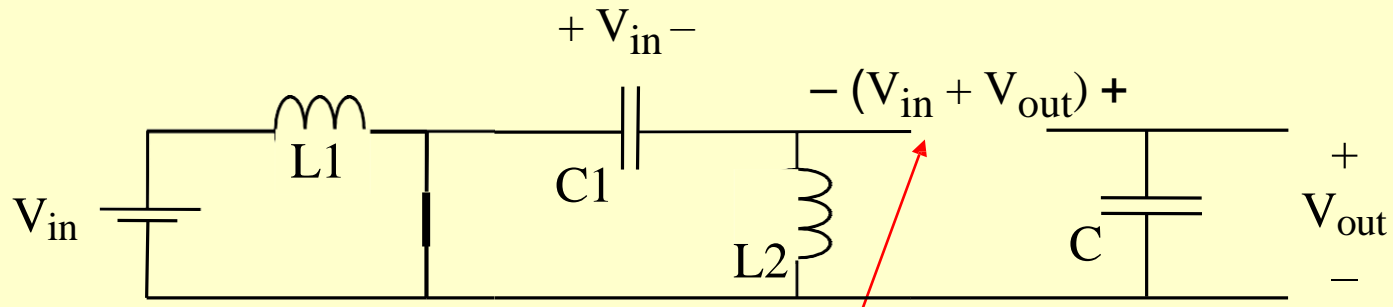


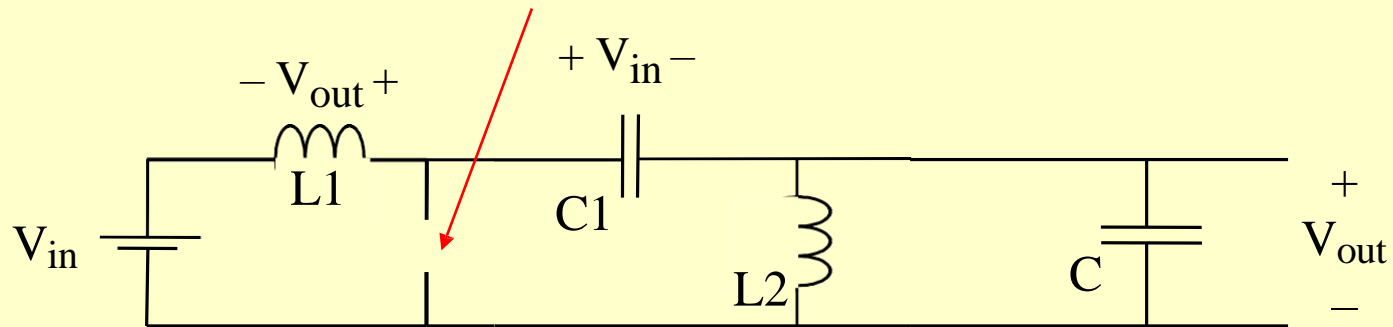MOSFET and diode see $(V_{in} + V_{out})$



- Diode and MOSFET, use $2(V_{in} + V_{out})$
- Capacitor $C1$, use $1.5V_{in}$
- Capacitor C , use $1.5V_{out}$

Continuous current in L1

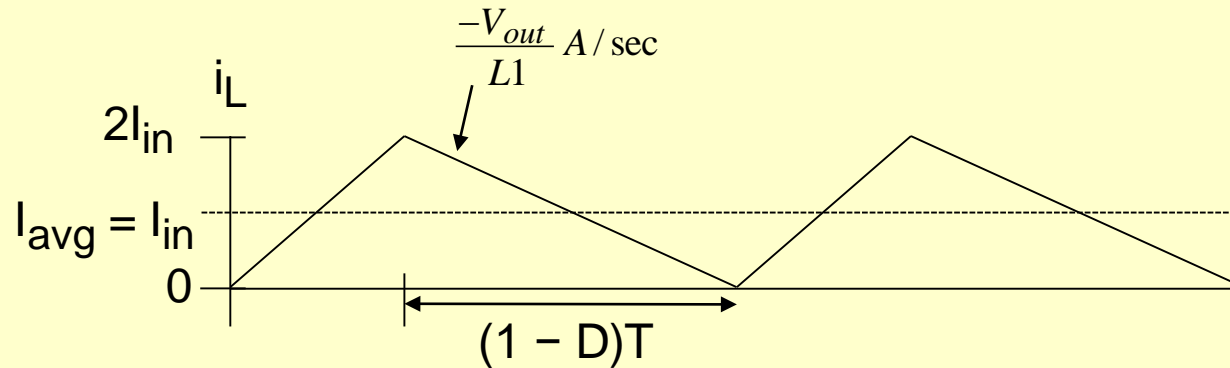

$$2I_{in} = \frac{V_{out}}{L1_{boundary}} \cdot (1-D)T = \frac{\frac{DV_{in}}{1-D}}{L1_{boundary}} \cdot (1-D)T = \frac{V_{in}D}{L1_{boundary}f}$$


$$L1_{boundary} = \frac{V_{in}D}{2I_{in}f}$$

Then, considering the worst case (i.e., $D \rightarrow 1$),

$$L1 > \frac{V_{in}}{2I_{in}f} \quad \text{guarantees continuous conduction}$$

← use max
← use min

Continuous current in L2

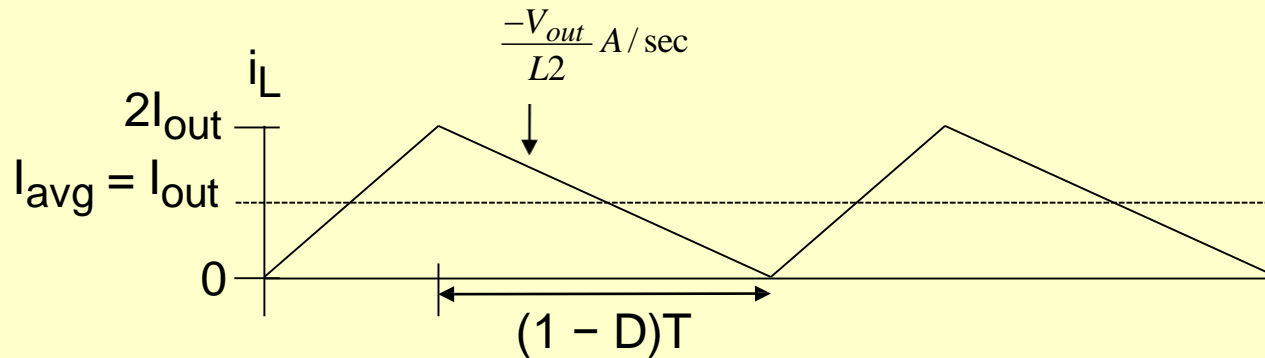

$$2I_{out} = \frac{V_{out}}{L2_{boundary}} \cdot (1-D)T = \frac{V_{out}(1-D)}{L2_{boundary} f}$$



$$L2_{boundary} = \frac{V_{out}(1-D)}{2I_{out} f}$$

Then, considering the worst case (i.e., $D \rightarrow 0$),

$$L2 > \frac{V_{out}}{2I_{out} f} \text{ guarantees continuous conduction}$$

← use max
← use min

Impedance matching

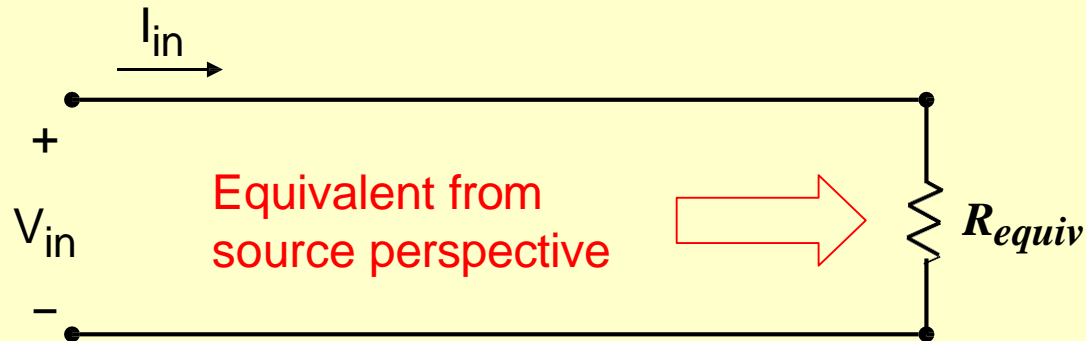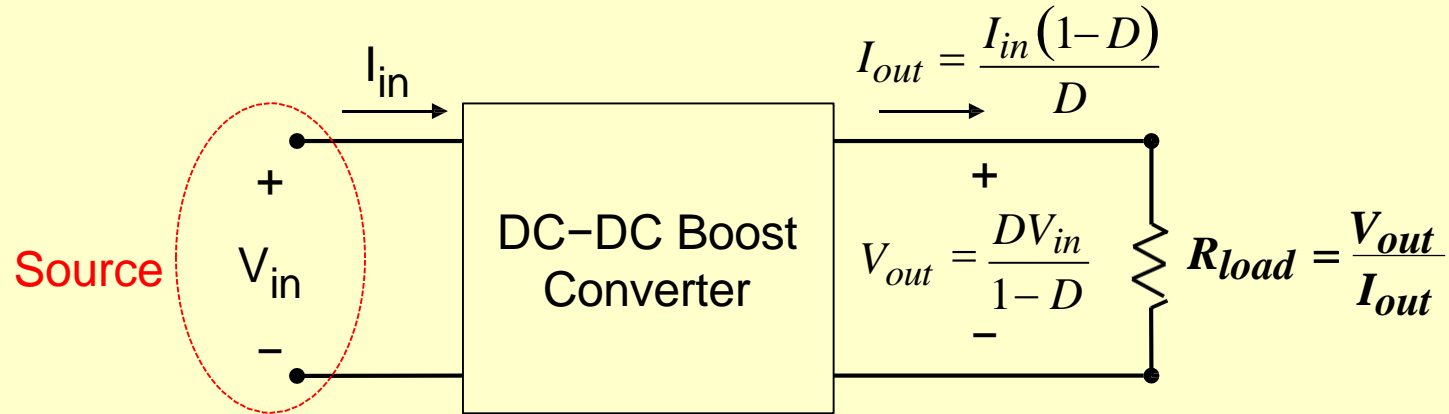

$$R_{equiv} = \frac{V_{in}}{I_{in}} = \frac{\frac{(1-D)V_{out}}{D}}{\frac{I_{out}}{(1-D)}} = \left(\frac{1-D}{D}\right)^2 \cdot \frac{V_{out}}{I_{out}} = \left(\frac{1-D}{D}\right)^2 R_{load}$$



Impedance matching


$$R_{equiv} = \frac{V_{in}}{I_{in}} = \frac{\frac{(1-D)V_{out}}{D}}{\frac{DI_{out}}{(1-D)}} = \left(\frac{1-D}{D}\right)^2 \cdot \frac{V_{out}}{I_{out}} = \left(\frac{1-D}{D}\right)^2 R_{load}$$

For any R_{load} , as $D \rightarrow 0$, then $R_{equiv} \rightarrow \infty$ (i.e., an open circuit)

For any R_{load} , as $D \rightarrow 1$, then $R_{equiv} \rightarrow 0$ (i.e., a short circuit)


Thus, the SEPIC converter can sweep the entire I-V curve of a solar panel

Example - connect a 100Ω load resistor

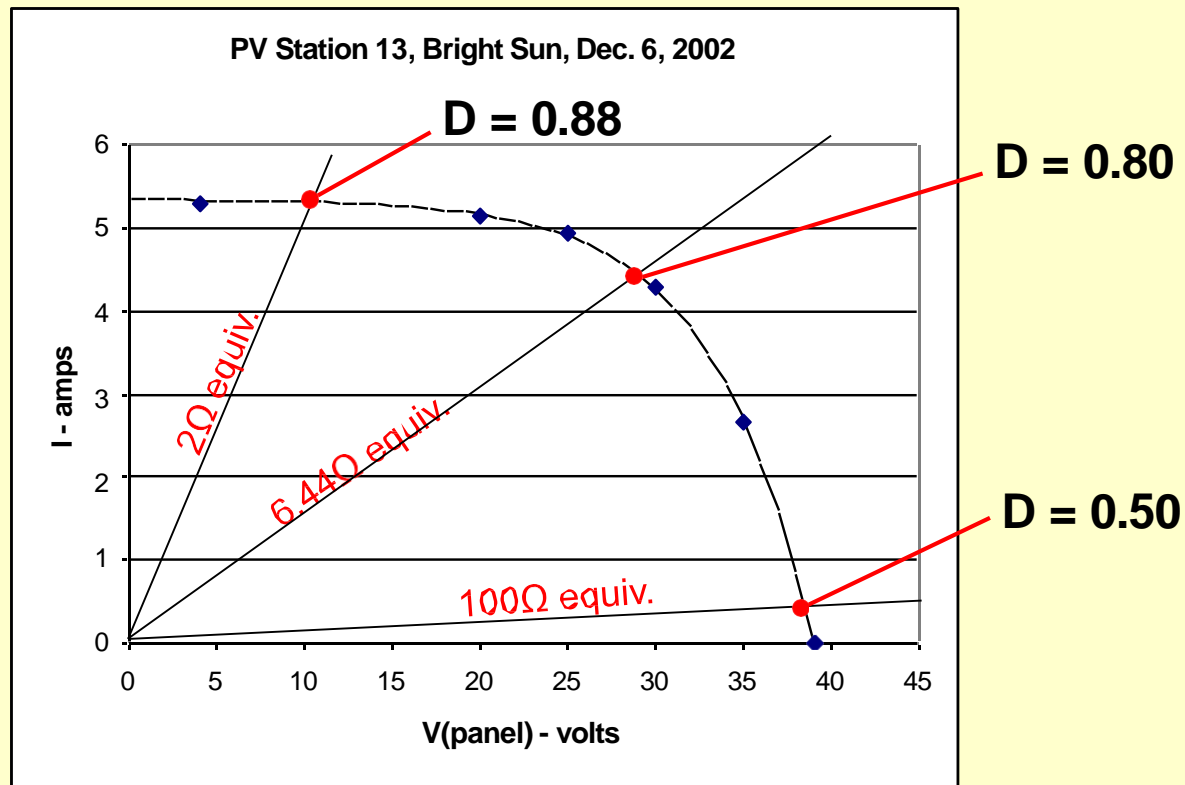

With a 100Ω load resistor attached, raising D from 0 to 1 moves the solar panel load from the open circuit condition to the short circuit condition

Example - connect a 5Ω load resistor

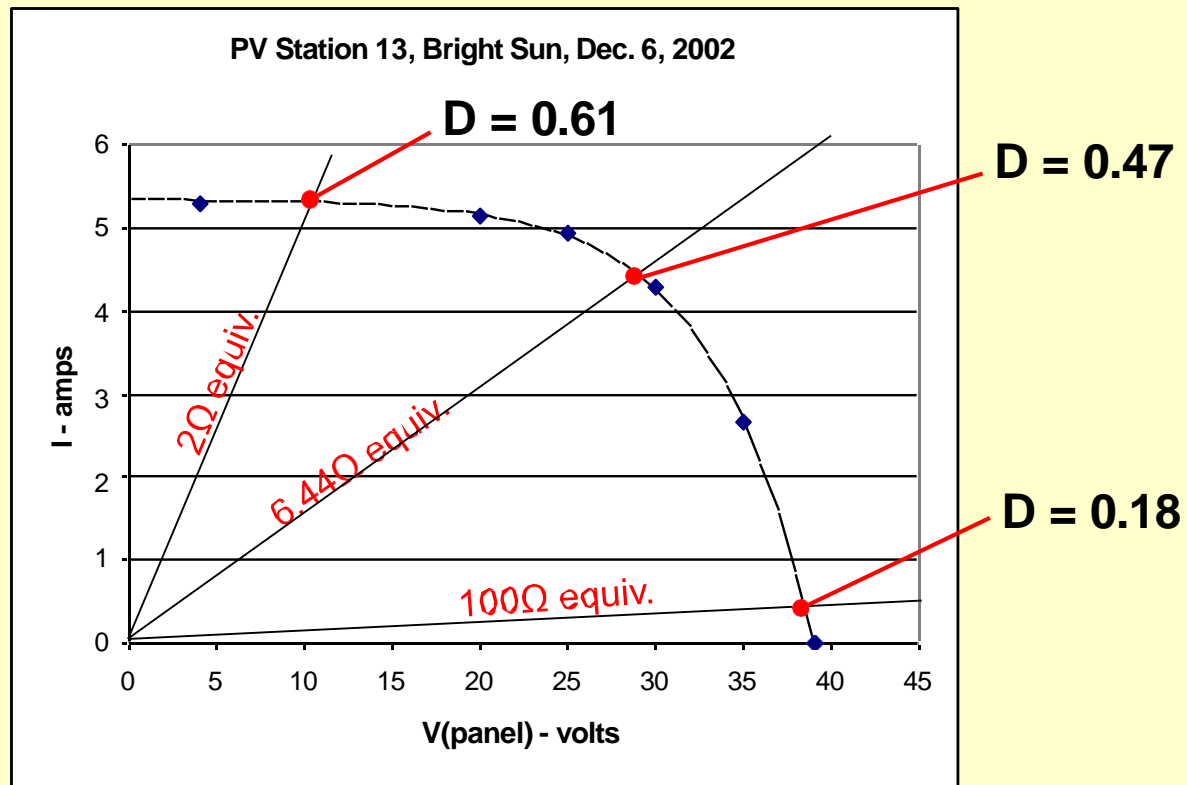

SEPIC DESIGN

Worst-Case Component Ratings Comparisons for DC-DC Converters

Our components

	9A	250V	5.66A p-p	200V, 250V	16A, 20A
Converter Type	Input Inductor Current (Arms)	Output Capacitor Voltage	Output Capacitor Current (Arms)	Diode and MOSFET Voltage	Diode and MOSFET Current (Arms)
Buck/Boost	$\frac{2}{\sqrt{3}} I_{in}$	$1.5V_{out}$	$\max \left(\frac{2}{\sqrt{3}} I_{in}, I_{out} \right)$	$2(V_{in} + V_{out})$	$\frac{2}{\sqrt{3}} (I_{in} + I_{out})$
	10A	90V	10A, 5A	40V, 90V	10A, 5A

Likely worst-case SEPIC situation

L1. 100μH, 9A

L2. 100μH, 9A

C. 1500μF, 250V, 5.66A p-p

C1. 33μF, 50V, 14A p-p

Diode D. 200V, 16A

MOSFET M. 250V, 20A

SEPIC DESIGN

Comparisons of Output Capacitor Ripple Voltage

Converter Type	Volts (peak-to-peak)
Buck/Boost	$\frac{I_{out}}{C_f}$

Annotations for the table above:

- A blue arrow points from the text **0.067V** to the fraction $\frac{I_{out}}{C_f}$.
- A red arrow points from the text **5A** to the I_{out} term in the numerator.
- Two red arrows point from the text **1500μF** and **50kHz** to the C_f term in the denominator.

L1. 100μH, 9A

C. 1500μF, 250V, 5.66A p-p

Diode D. 200V, 16A

MOSFET M. 250V, 20A

L2. 100μH, 9A

C1. 33μF, 50V, 14A p-p

SEPIC DESIGN

Minimum Inductance Values Needed to Guarantee Continuous Current

Converter Type	For Continuous Current in the Input Inductor	For Continuous Current in L2
Buck/Boost	$L_1 > \frac{V_{in}}{2I_{in}f}$ <p> $V_{in} = 40V$ $I_{in} = 2A$ $f = 50kHz$ $L_1 = 200\mu H$ </p>	$L_2 > \frac{V_{out}}{2I_{out}f}$ <p> $V_{out} = 90V$ $I_{out} = 2A$ $f = 50kHz$ $L_2 = 450\mu H$ </p>

L1. 100μH, 9A

C. 1500μF, 250V, 5.66A p-p

Diode D. 200V, 16A

MOSFET M. 250V, 20A

L2. 100μH, 9A

C1. 33μF, 50V, 14A p-p

SEPIC DESIGN

Additional Components for SEPIC converter

50V	14A p-p	Our components	9A
Series Capacitor Voltage	Series Capacitor (C ₁) Current (Arms)	Series Capacitor (C ₁) Ripple Voltage (peak-to-peak)	Second Inductor (L ₂) Current (Arms)
$1.5V_{in}$	$\max\left(\frac{2}{\sqrt{3}} I_{in}, \frac{2}{\sqrt{3}} I_{out}\right)$	$\frac{I_{out}}{C_1 f}$ ← 5A 3.0V	$\frac{2}{\sqrt{3}} I_{out}$
40V	10A	5A	5A
		33μF	50kHz

Likely worst-case SEPIC situation

L1. 100μH, 9A

L2. 100μH, 9A

C. 1500μF, 250V, 5.66A p-p

C1. 33μF, 50V, 14A p-p

Diode D. 200V, 16A

Conclusion - 50kHz may be too low for SEPIC converter

MOSFET M. 250V, 20A