

15A05402:COMPUTER ORGANISATION

# Integer Multipliers

S BABU

AP/CSE

KEC.

# Basic Arithmetic and the ALU

- Earlier in the semester
  - Number representations, 2's complement, unsigned
  - Addition/Subtraction
  - Add/Sub ALU
    - Full adder, ripple carry, subtraction
  - Carry-lookahead addition
  - Logical operations
    - and, or, xor, nor, shifts
  - Overflow

# Basic Arithmetic and the ALU

- Now
  - Integer multiplication
    - Booth's algorithm
- This is not crucial for the project

# Multiplication


- Flashback to 3<sup>rd</sup> grade
  - Multiplier
  - Multiplicand
  - Partial products
  - Final sum
- Base 10:  $8 \times 9 = 72$ 
  - PP:  $8 + 0 + 0 + 64 = 72$
- How wide is the result?
  - $\log(n \times m) = \log(n) + \log(m)$
  - $32b \times 32b = 64b$  result

$$\begin{array}{r} 1000 \\ \times 1001 \\ \hline 1000 \\ 0000 \\ 0000 \\ 1000 \\ \hline 1001000 \end{array}$$


# Array Multiplier

				1	0	0	0				
				x	1	0	0	1			
					1	0	0	0			
					0	0	0	0			
					0	0	0	0			
					0	0	0	0			
					1	0	0	0			
					1	0	0	1	0	0	0

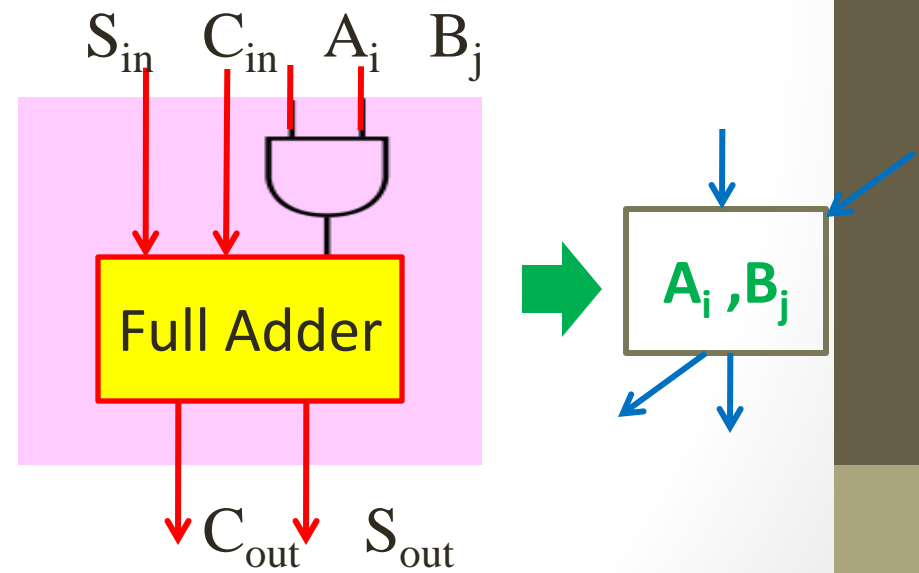- Adding all partial products simultaneously using an array of basic cells



# 16-bit Array Multiplier

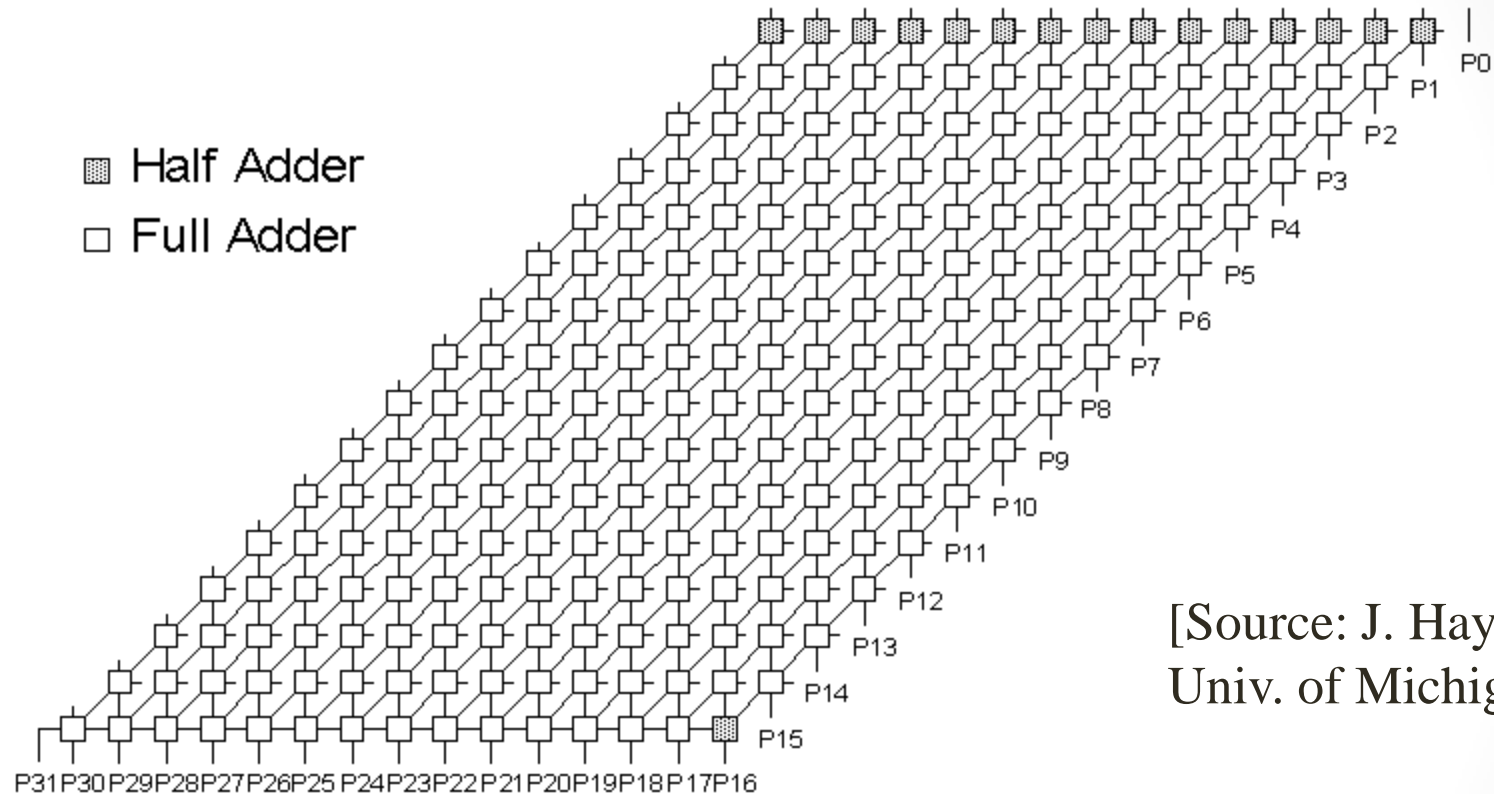

[Source: J. Hayes,  
Univ. of Michigan]

Conceptually straightforward

Fairly expensive hardware, integer multiplies relatively rare


Most used in array address calc: replace with shifts

# Instead: Multicycle Multipliers

- Combinational multipliers
  - Very hardware-intensive
  - Integer multiply relatively rare
  - Not the right place to spend resources
- Multicycle multipliers
  - Iterate through bits of multiplier
  - Conditionally add shifted multiplicand
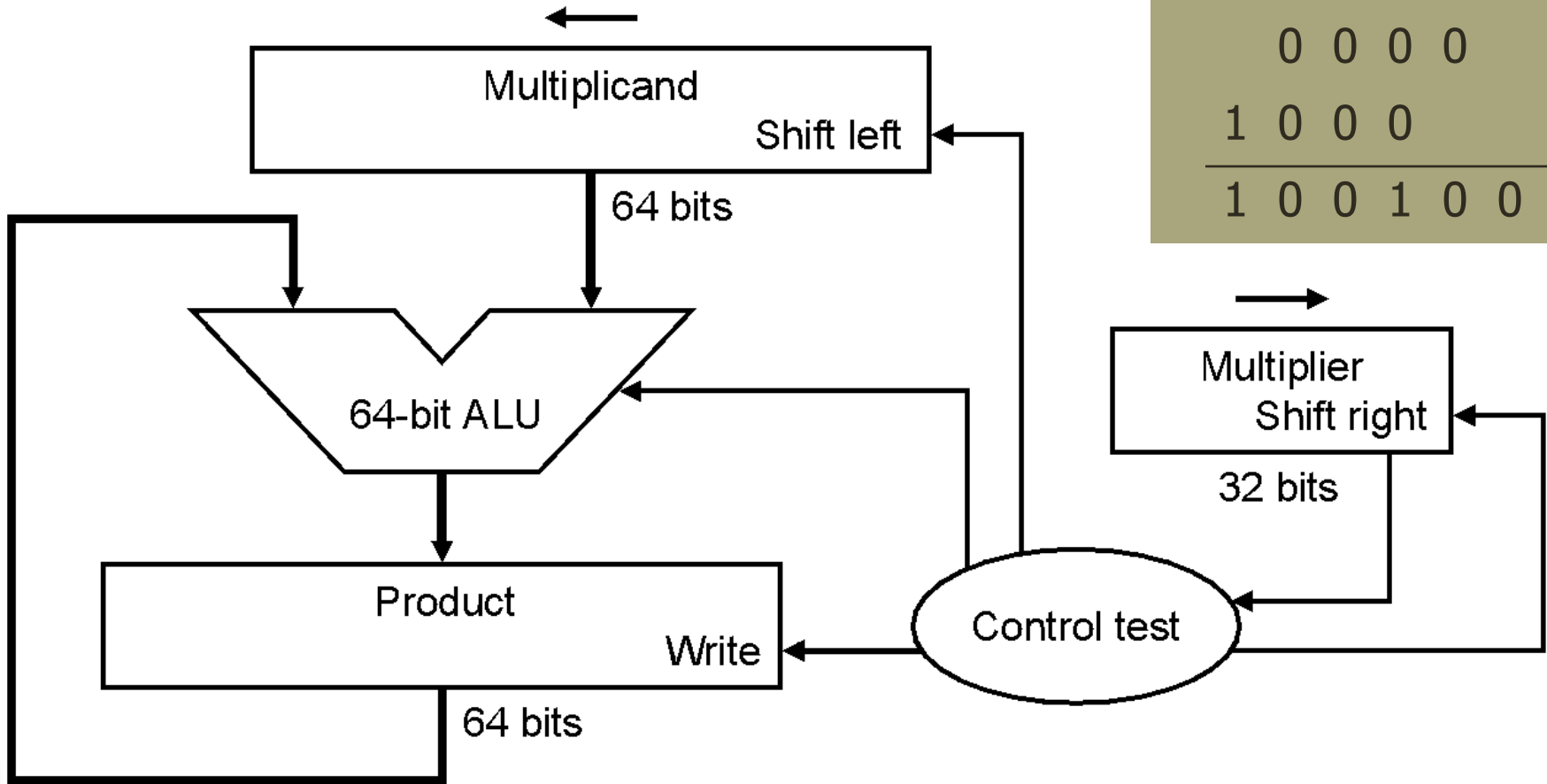
# Multiplier


$$\begin{array}{r} 1000 \\ \times 1001 \\ \hline 1000 \\ 0000 \\ 0000 \\ 1000 \\ \hline 1001000 \end{array}$$




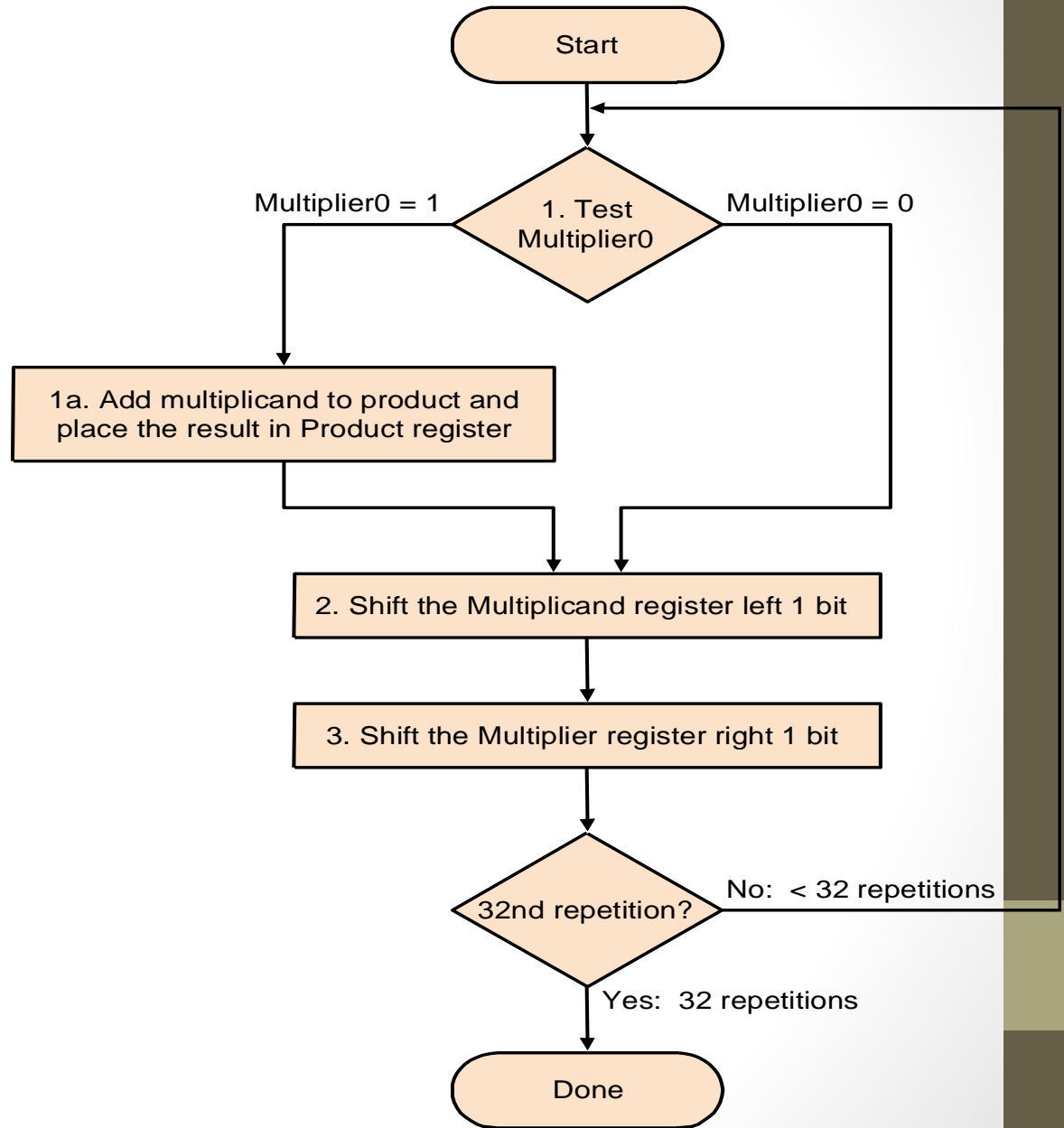
# Multiplier


```
      1 0 0 0
    x 1 0 0 1
  -----
      1 0 0 0
     0 0 0 0
    0 0 0 0
   1 0 0 0
  -----
  1 0 0 1 0 0 0
```



# Multiplier Improvements

- Do we really need a 64-bit adder?
  - No, since low-order bits are not involved
  - Hence, just use a 32-bit adder
    - Shift product register right on every step
- Do we really need a separate multiplier register?
  - No, since low-order bits of 64-bit product are initially unused
  - Hence, just store multiplier there initially


# Multiplier

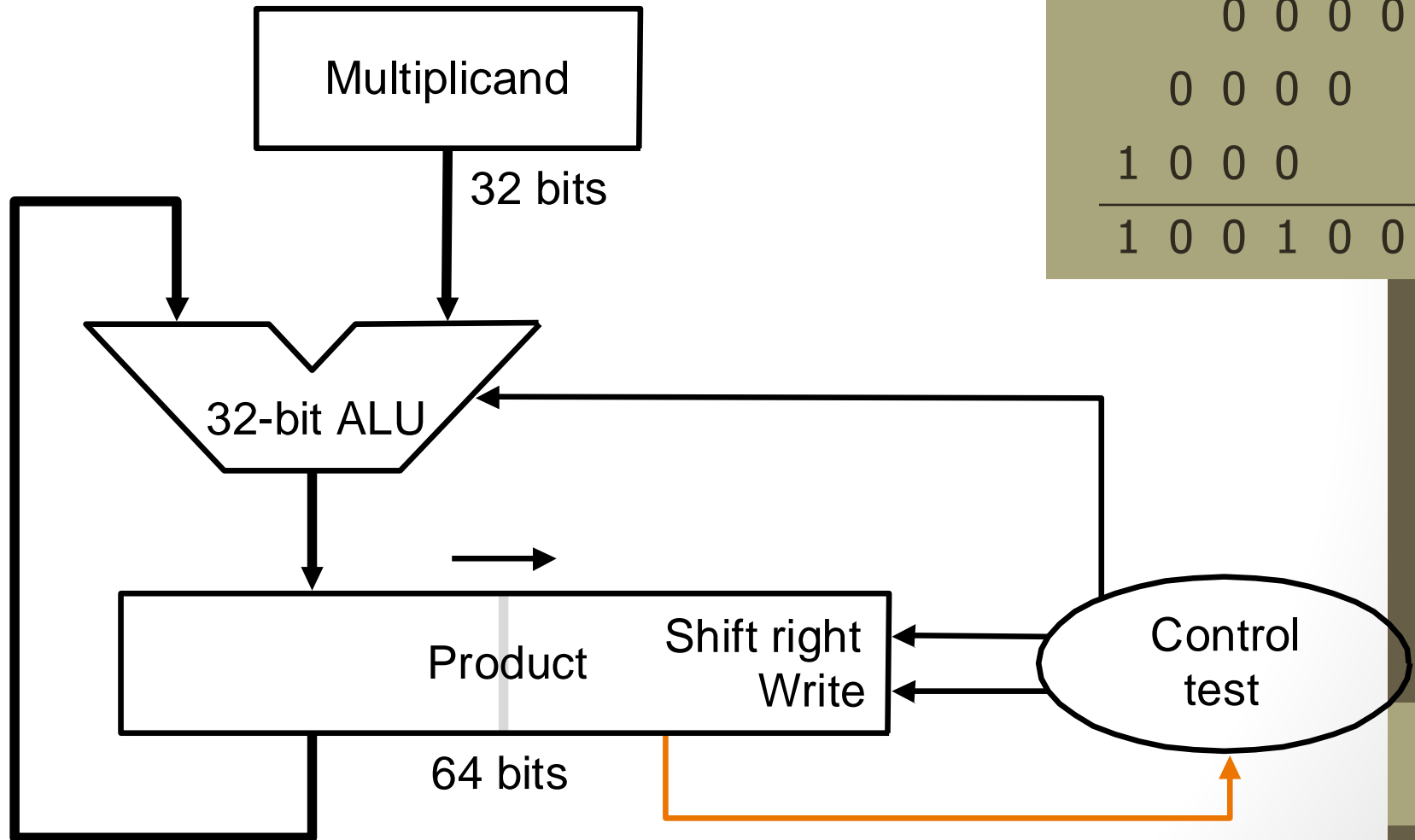

```
      1 0 0 0
    x 1 0 0 1
    -----
      1 0 0 0
    0 0 0 0
  0 0 0 0
1 0 0 0
-----
1 0 0 1 0 0 0
```
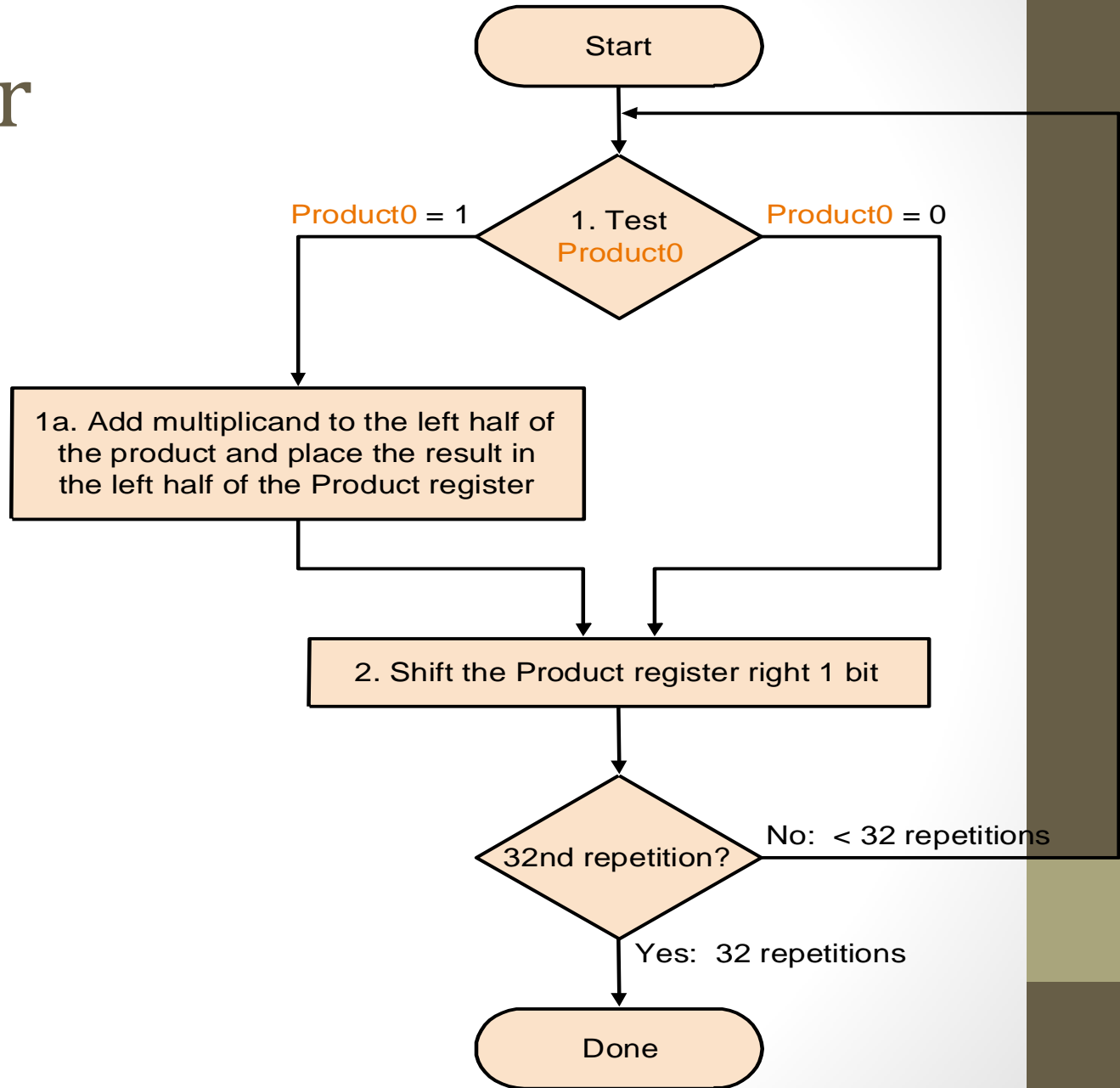
# Multiplier

```
      1 0 0 0
    x 1 0 0 1
  -----
      1 0 0 0
     0 0 0 0
    0 0 0 0
   1 0 0 0
  -----
  1 0 0 1 0 0 0
```



# Signed Multiplication

- Recall
  - For  $p = a \times b$ , if  $a < 0$  or  $b < 0$ , then  $p < 0$
  - If  $a < 0$  and  $b < 0$ , then  $p > 0$
  - Hence  $\text{sign}(p) = \text{sign}(a) \text{ xor } \text{sign}(b)$
- Hence
  - Convert multiplier, multiplicand to positive number with  $(n-1)$  bits
  - Multiply positive numbers
  - Compute sign, convert product accordingly
- Or,
  - Perform sign-extension on shifts for prev. design
  - Right answer falls out

# Booth's Encoding

- Recall grade school trick
  - When multiplying by 9:
    - Multiply by 10 (easy, just shift digits left)
    - Subtract once
  - E.g.
    - $123454 \times 9 = 123454 \times (10 - 1) = 1234540 - 123454$
    - Converts addition of six partial products to one shift and one subtraction
- Booth's algorithm applies same principle
  - Except no '9' in binary, just '1' and '0'
  - So, it's actually easier!

# Booth's Encoding

- Search for a run of '1' bits in the multiplier
  - E.g. '0110' has a run of 2 '1' bits in the middle
  - Multiplying by '0110' (6 in decimal) is equivalent to multiplying by 8 and subtracting twice, since  $6 \times m = (8 - 2) \times m = 8m - 2m$
- Hence, iterate right to left and:
  - Subtract multiplicand from product at first '1'
  - Add multiplicand to product after last '1'
  - Don't do either for '1' bits in the middle

# Booth's Algorithm

Current bit	Bit to right	Explanation	Example	Operation
1	0	Begins run of '1'	0000111 <b>1</b> 000	Subtract
1	1	Middle of run of '1'	000011 <b>11</b> 000	Nothing
0	1	End of a run of '1'	000 <b>01</b> 111000	Add
0	0	Middle of a run of '0'	0 <b>00</b> 01111000	Nothing



# Booth's Encoding

- Really just a new way to encode numbers
  - Normally positionally weighted as  $2^n$
  - With Booth, each position has a sign bit
  - Can be extended to multiple bits

0	1	1	0	Binary
+1	0	-1	0	1-bit Booth
+2		-2		2-bit Booth

# 2-bits/cycle Booth Multiplier

- For every pair of multiplier bits
  - If Booth's encoding is '-2'
    - Shift multiplicand left by 1, then subtract
  - If Booth's encoding is '-1'
    - Subtract
  - If Booth's encoding is '0'
    - Do nothing
  - If Booth's encoding is '1'
    - Add
  - If Booth's encoding is '2'
    - Shift multiplicand left by 1, then add

# 2 bits/cycle Booth's

1 bit Booth	
00	+0
01	+M;
10	-M;
11	+0

Current	Previous	Operation	Explanation
<u>00</u>	0	+0; shift 2	[00] => +0, [00] => +0; $2x(+0) + (+0) = +0$
<u>00</u>	1	+M; shift 2	[00] => +0, [01] => +M; $2x(+0) + (+M) = +M$
<u>01</u>	0	+M; shift 2	[01] => +M, [10] => -M; $2x(+M) + (-M) = +M$
<u>01</u>	1	+2M; shift 2	[01] => +M, [11] => +0; $2x(+M) + (+0) = +2M$
<u>10</u>	0	-2M; shift 2	[10] => -M, [00] => +0; $2x(-M) + (+0) = -2M$
<u>10</u>	1	-M; shift 2	[10] => -M, [01] => +M; $2x(-M) + (+M) = -M$
<u>11</u>	0	-M; shift 2	[11] => +0, [10] => -M; $2x(+0) + (-M) = -M$
<u>11</u>	1	+0; shift 2	[11] => +0, [11] => +0; $2x(+0) + (+0) = +0$

# Booth's Example

- Negative multiplicand:

$$-6 \times 6 = -36$$

1010 x 0110, 0110 in Booth's encoding is +0-0

Hence:

1111 1010	x 0	0000 0000
1111 0100	x -1	0000 1100
1110 1000	x 0	0000 0000
1101 0000	x +1	1101 0000
	Final Sum:	1101 1100 (-36)

# Booth's Example

- Negative multiplier:

$$-6 \times -2 = 12$$

1010 x 1110, 1110 in Booth's encoding is 00-0

Hence:

1111 1010	x 0	0000 0000
1111 0100	x -1	0000 1100
1110 1000	x 0	0000 0000
1101 0000	x 0	0000 0000
	Final Sum:	0000 1100 (12)

# Summary

- Integer multiply
  - Combinational
  - Multicycle
  - Booth's algorithm