

Pipelining

- Pipelining is a general-purpose efficiency technique
 - It is not specific to processors
- Pipelining is used in:
 - Assembly lines
 - Bucket brigades
 - Fast food restaurants
- Pipelining is used in other CS disciplines:
 - Networking
 - Server software architecture
- Useful to increase throughput in the presence of long latency
 - More on that later...

Pipelining Processors

- We've seen two possible implementations of the MIPS architecture.
 - A **single-cycle datapath** executes each instruction in just one clock cycle, but the cycle time may be very long.
 - A **multicycle datapath** has much shorter cycle times, but each instruction requires many cycles to execute.
- **Pipelining** gives the best of both worlds and is used in just about every modern processor.
 - Cycle times are short so clock rates are high.
 - But we can still execute an instruction in about one clock cycle!

Single Cycle Datapath	CPI = 1	Long Cycle Time
Multi-cycle Datapath	CPI = ~4	Short Cycle Time
Pipelined Datapath	CPI = ~1	Short Cycle Time

Instruction execution review


- Executing a MIPS instruction can take up to five steps.

Step	Name	Description
Instruction Fetch	IF	Read an instruction from memory.
Instruction Decode	ID	Read source registers and generate control signals.
Execute	EX	Compute an R-type result or a branch outcome.
Memory	MEM	Read or write the data memory.
Writeback	WB	Store a result in the destination register.

- However, as we saw, not all instructions need all five steps.

Instruction	Steps required				
beq	IF	ID	EX		
R-type	IF	ID	EX		WB
sw	IF	ID	EX	MEM	
lw	IF	ID	EX	MEM	WB


Single-cycle datapath diagram

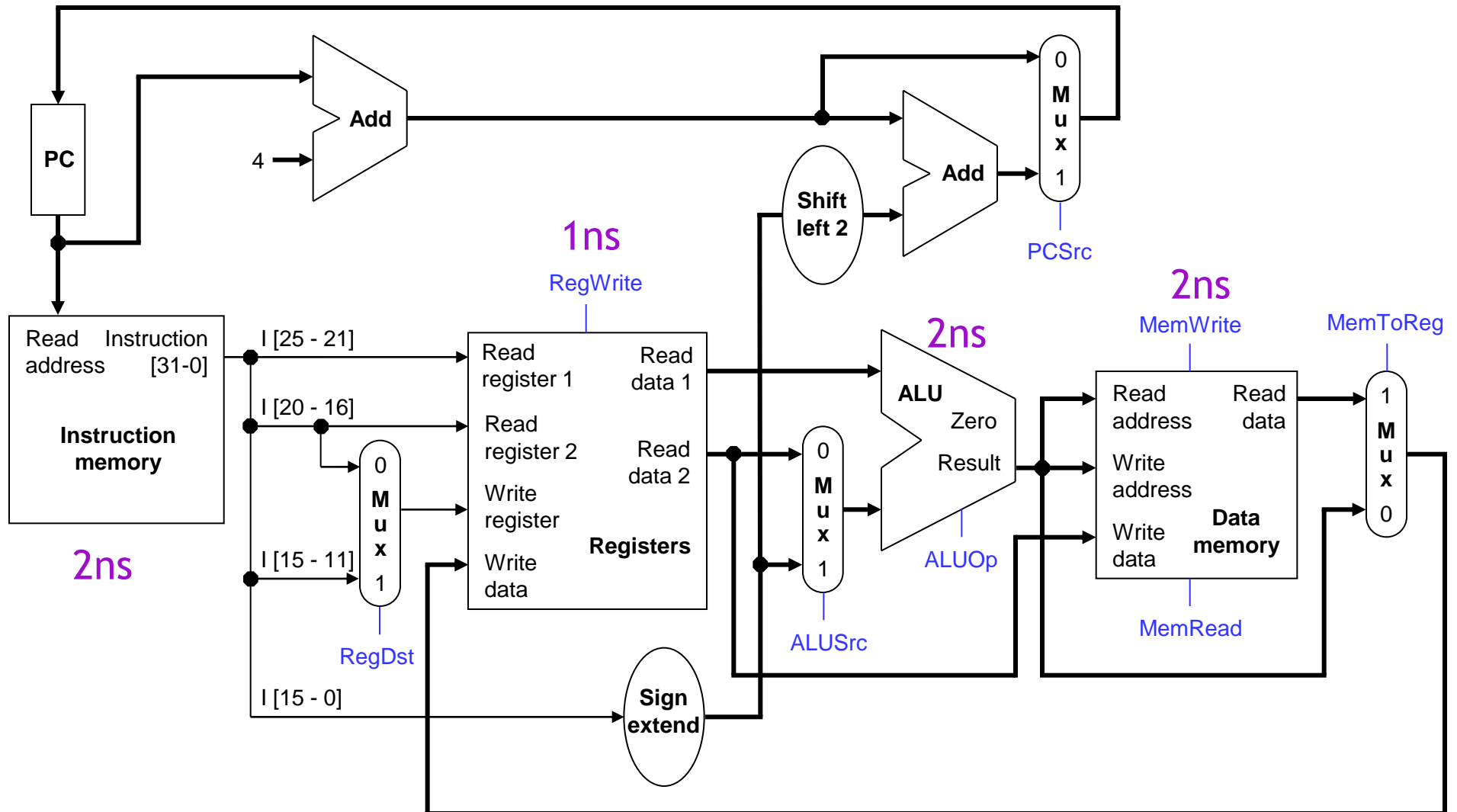

- How long does it take to execute each instruction?

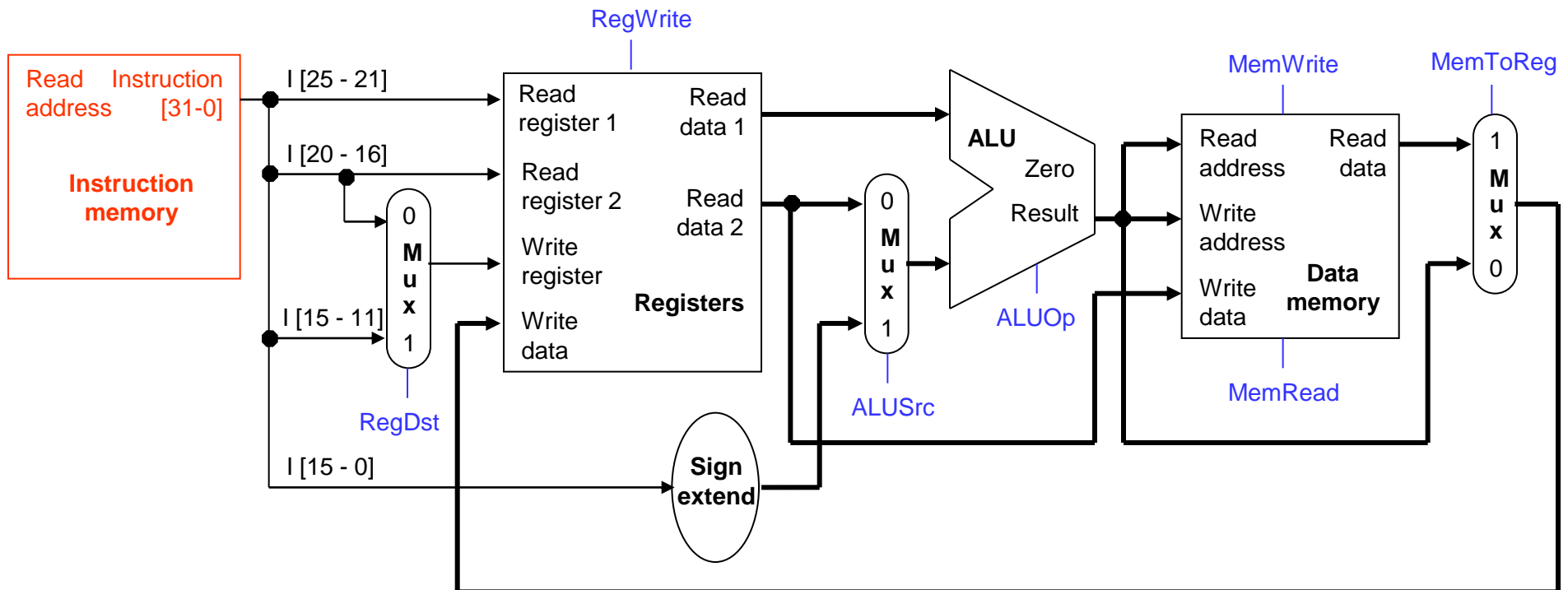
Example: Instruction Fetch (IF)

- Let's quickly review how `lw` is executed in the single-cycle datapath.
- We'll ignore PC incrementing and branching for now.
- In the Instruction Fetch (IF) step, we read the instruction memory.




Instruction Decode (ID)

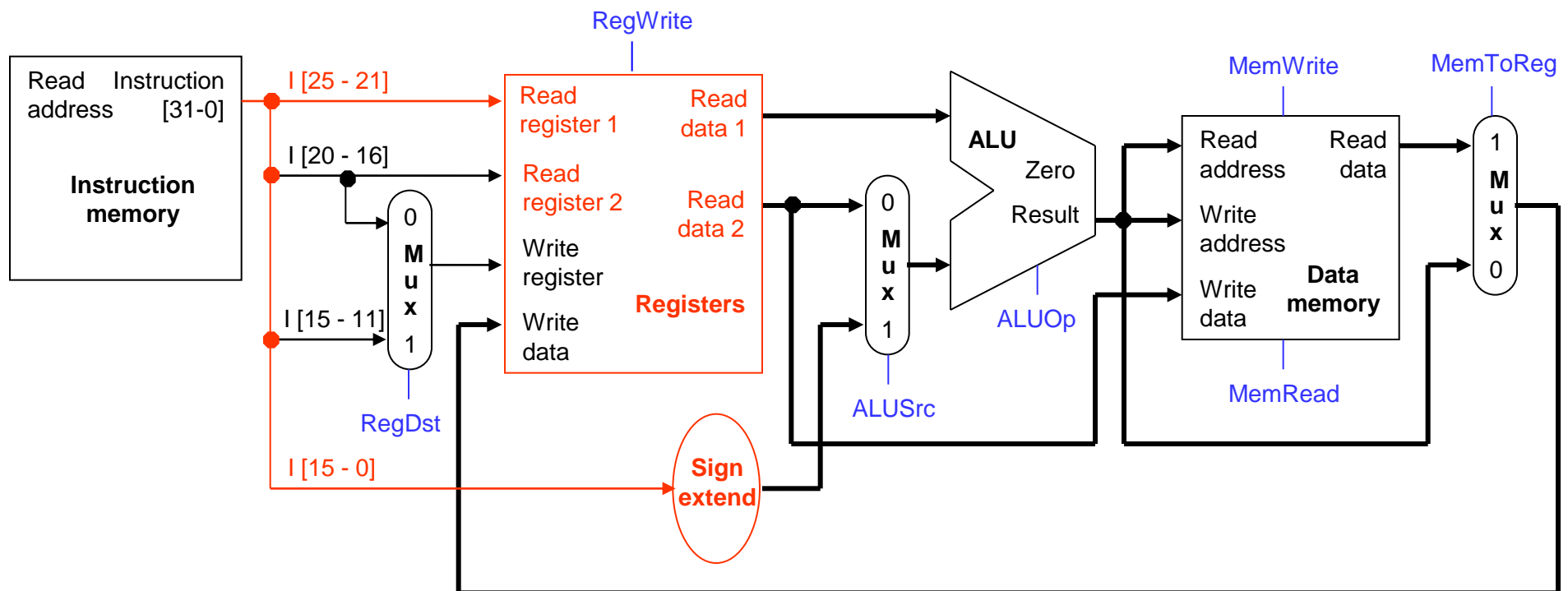- The Instruction Decode (ID) step reads the source register from the register file.




Execute (EX)

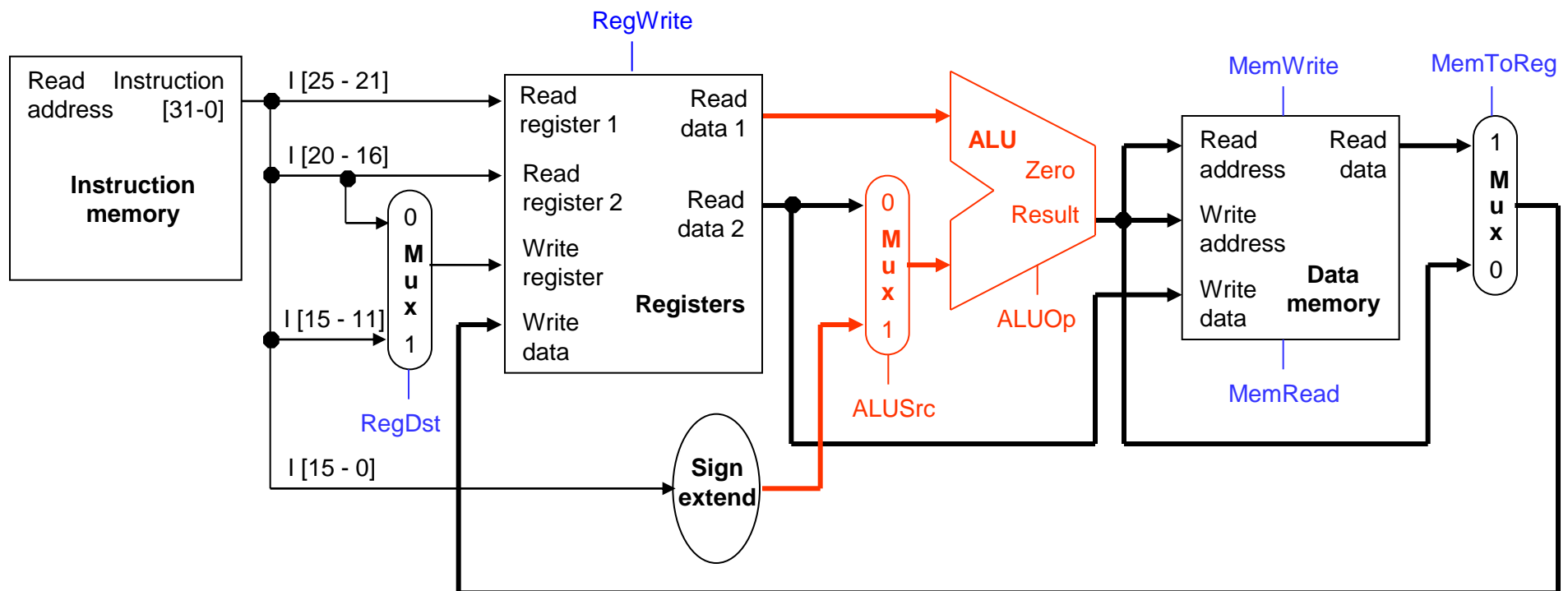- The third step, Execute (EX), computes the effective memory address from the source register and the instruction's constant field.




Memory (MEM)

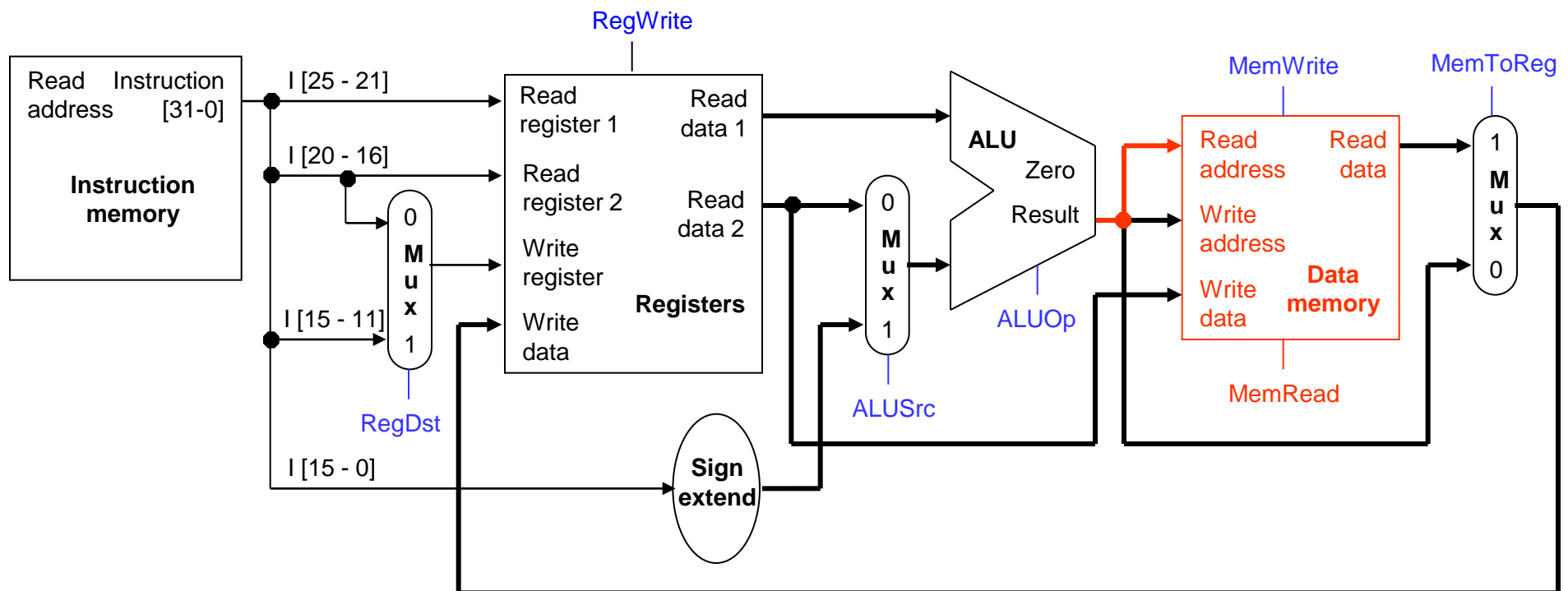- The Memory (MEM) step involves reading the data memory, from the address computed by the ALU.



Writeback (WB)

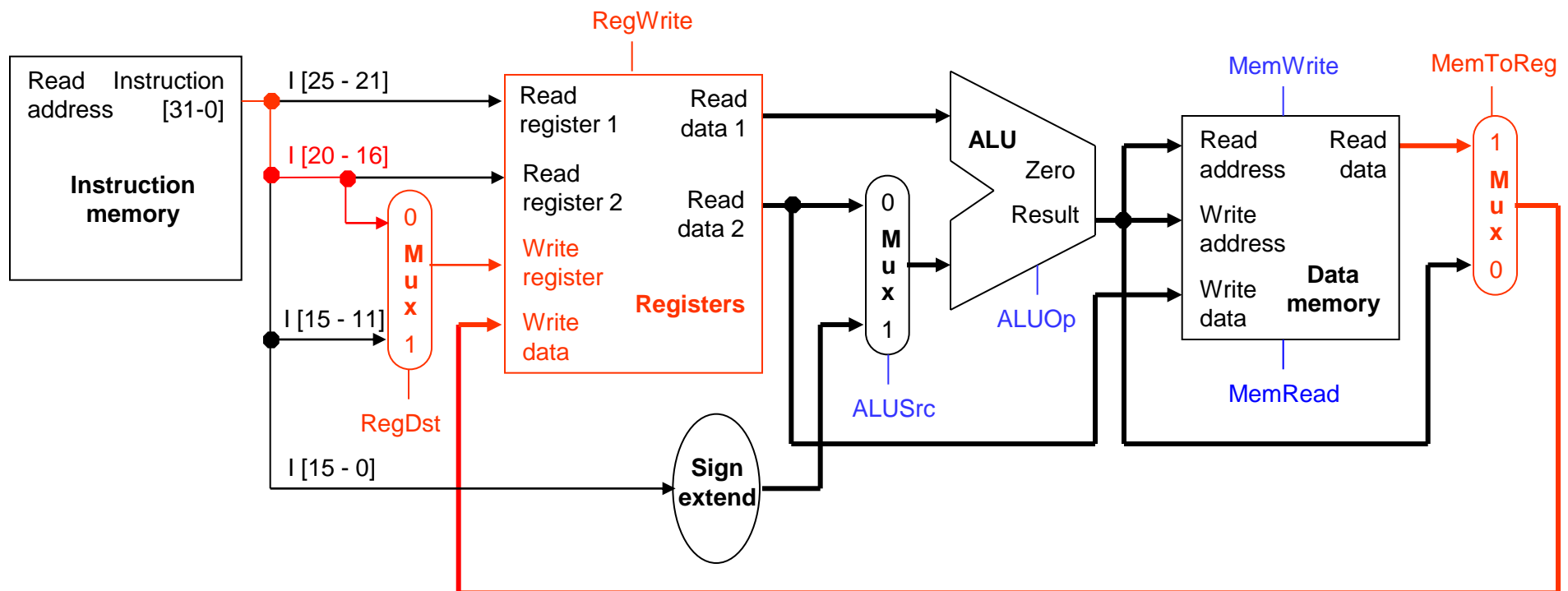- Finally, in the Writeback (WB) step, the memory value is stored into the destination register.




A bunch of lazy functional units

- Notice that each execution step uses a different functional unit.
- In other words, the main units are idle for most of the 8ns cycle!
 - The instruction RAM is used for just 2ns at the start of the cycle.
 - Registers are read once in ID (1ns), and written once in WB (1ns).
 - The ALU is used for 2ns near the middle of the cycle.
 - Reading the data memory only takes 2ns as well.
- That's a lot of hardware sitting around doing nothing.


Putting those slackers to work

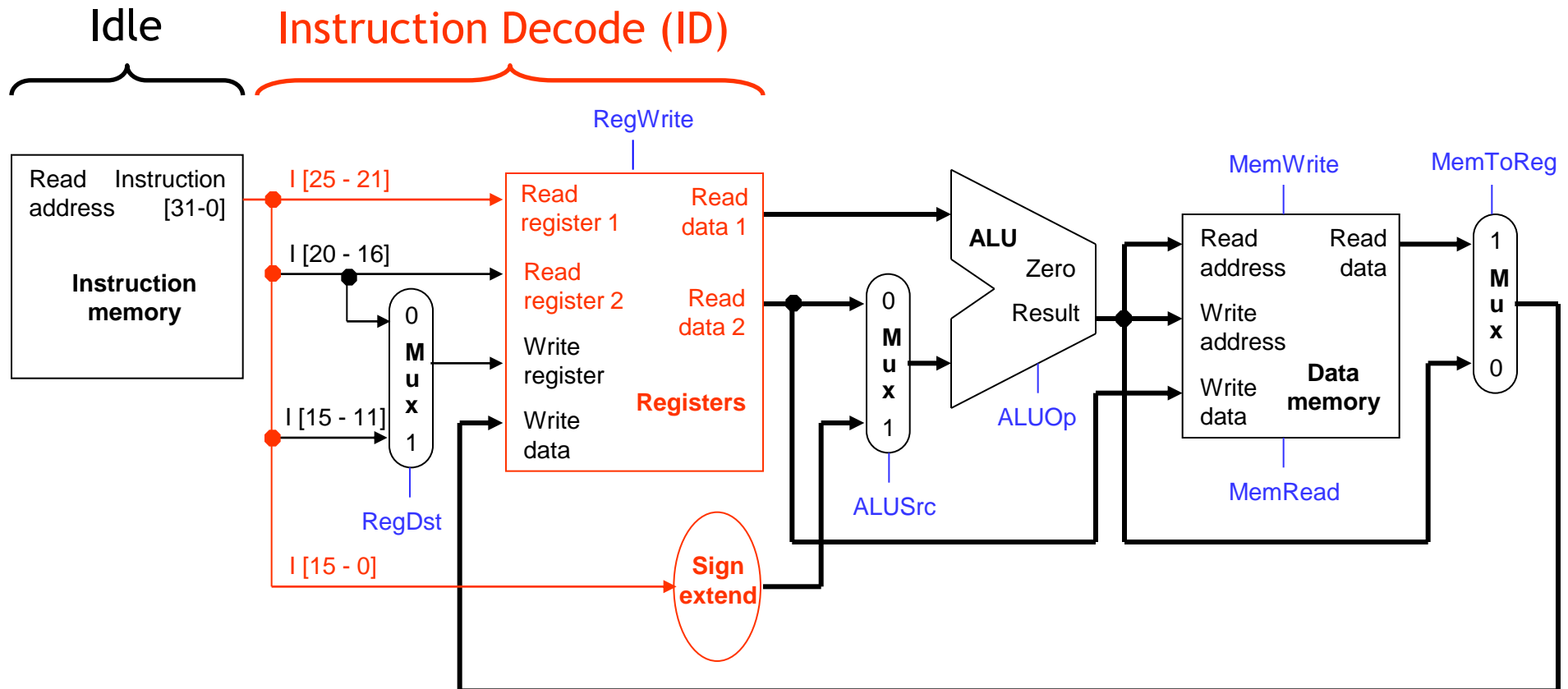- We shouldn't have to wait for the entire instruction to complete before we can re-use the functional units.
- For example, the instruction memory is free in the Instruction Decode step as shown below, so...




Decoding and fetching together

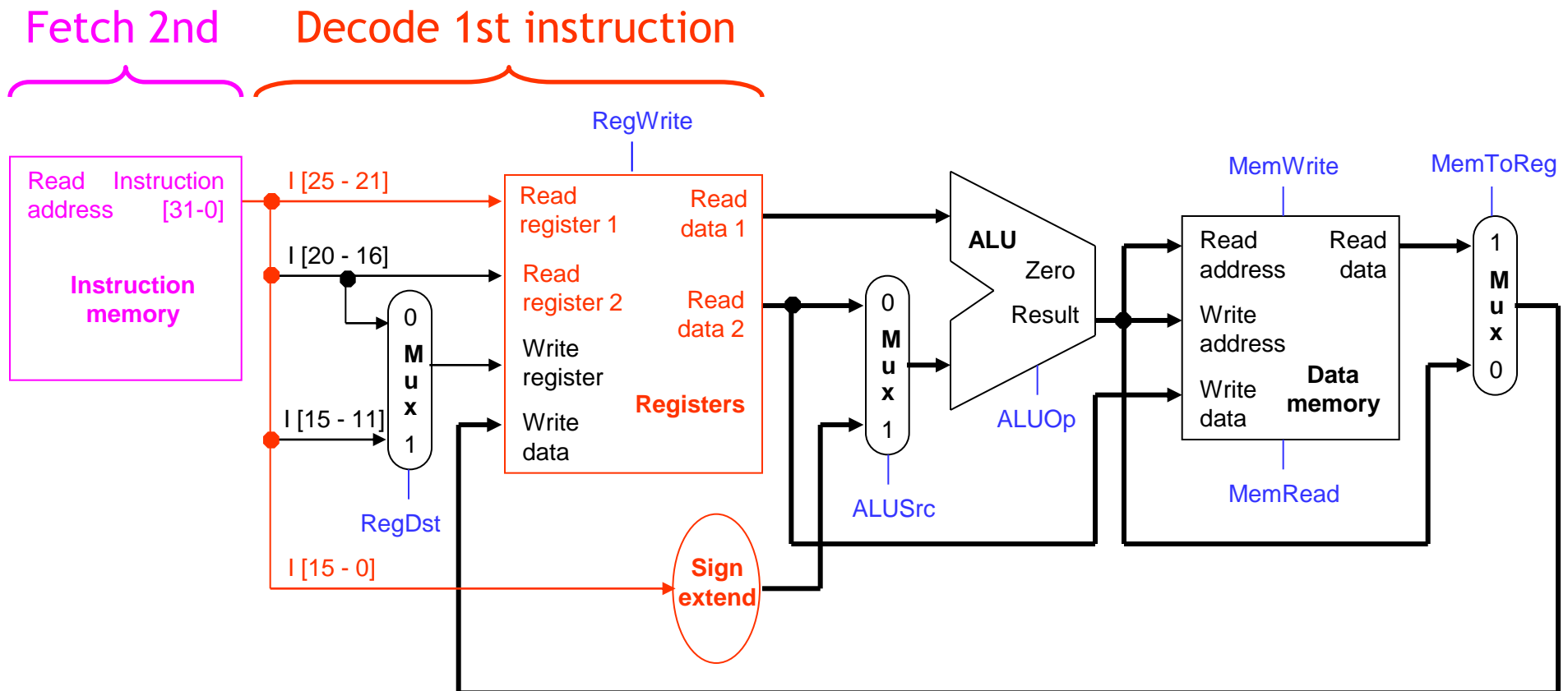- Why don't we go ahead and fetch the *next* instruction while we're decoding the first one?



Executing, decoding and fetching

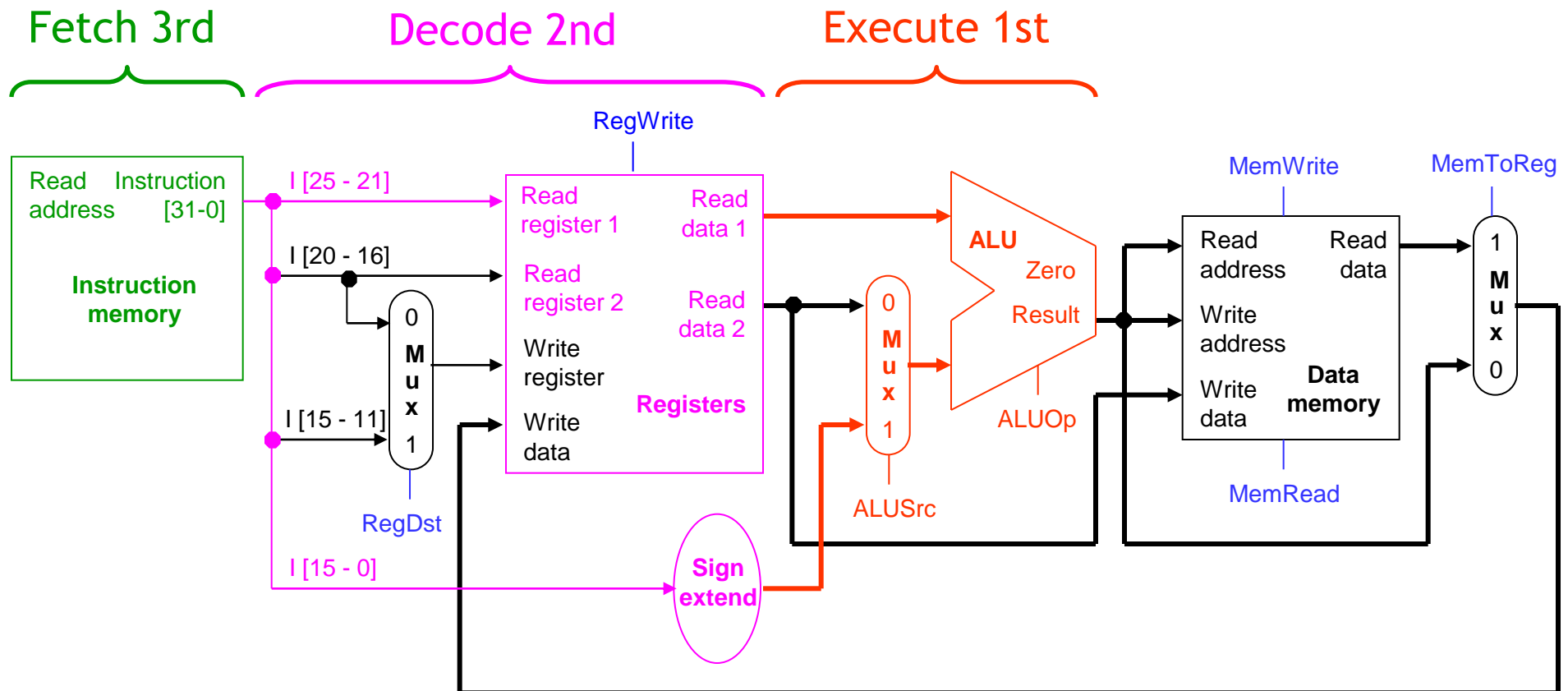- Similarly, once the first instruction enters its Execute stage, we can go ahead and decode the second instruction.
- But now the instruction memory is free again, so we can fetch the third instruction!




Making Pipelining Work

- We'll make our pipeline 5 stages long, to handle load instructions as they were handled in the multi-cycle implementation
 - Stages are: IF, ID, EX, MEM, and WB
- We want to support executing 5 instructions simultaneously: one in each stage.




Break datapath into 5 stages

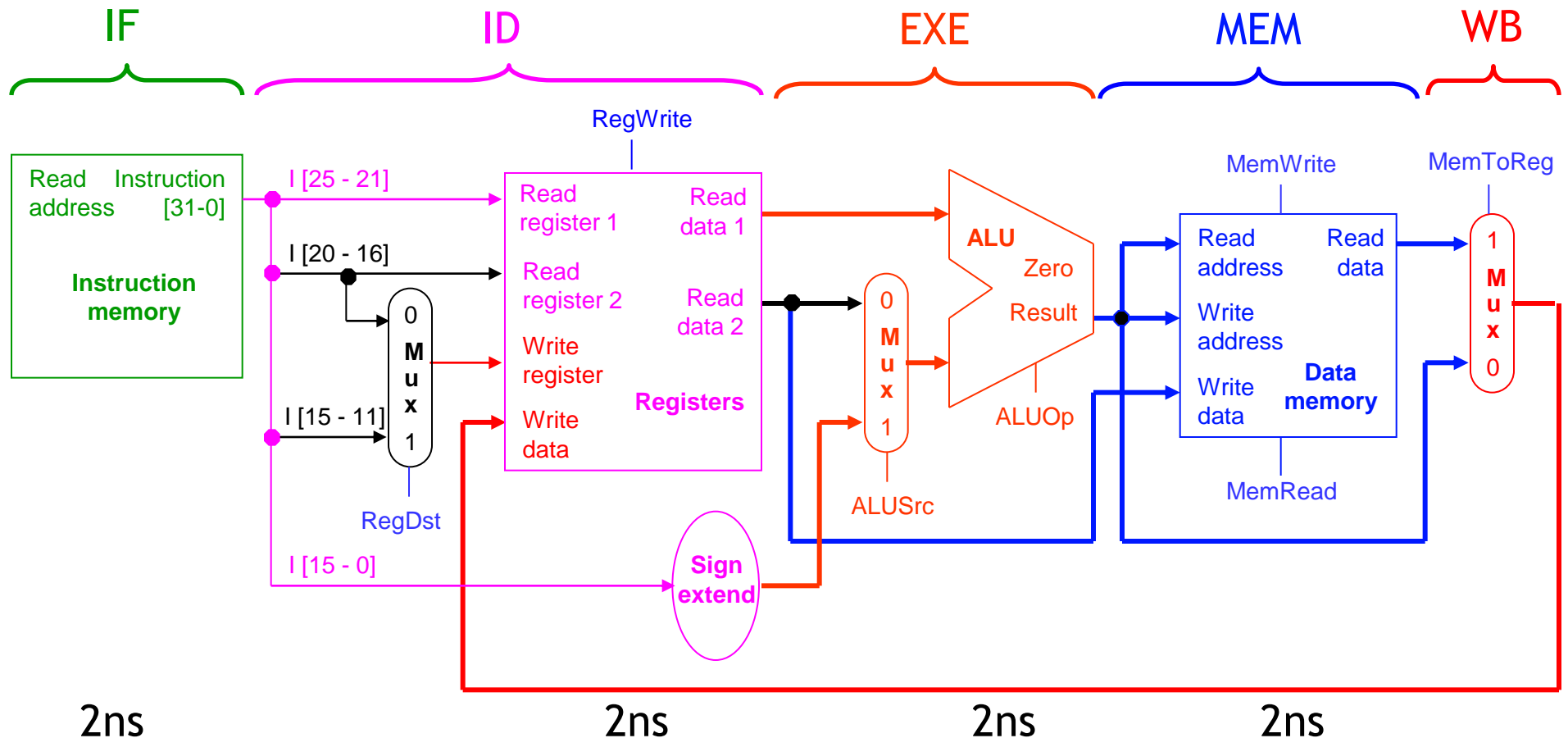- Each stage has its own functional units.
- Each stage can execute in 2ns
 - Just like the multi-cycle implementation




Pipelining Loads

		Clock cycle								
		1	2	3	4	5	6	7	8	9
lw	\$t0, 4(\$sp)	IF	ID	EX	MEM	WB				
lw	\$t1, 8(\$sp)		IF	ID	EX	MEM	WB			
lw	\$t2, 12(\$sp)			IF	ID	EX	MEM	WB		
lw	\$t3, 16(\$sp)				IF	ID	EX	MEM	WB	
lw	\$t4, 20(\$sp)					IF	ID	EX	MEM	WB

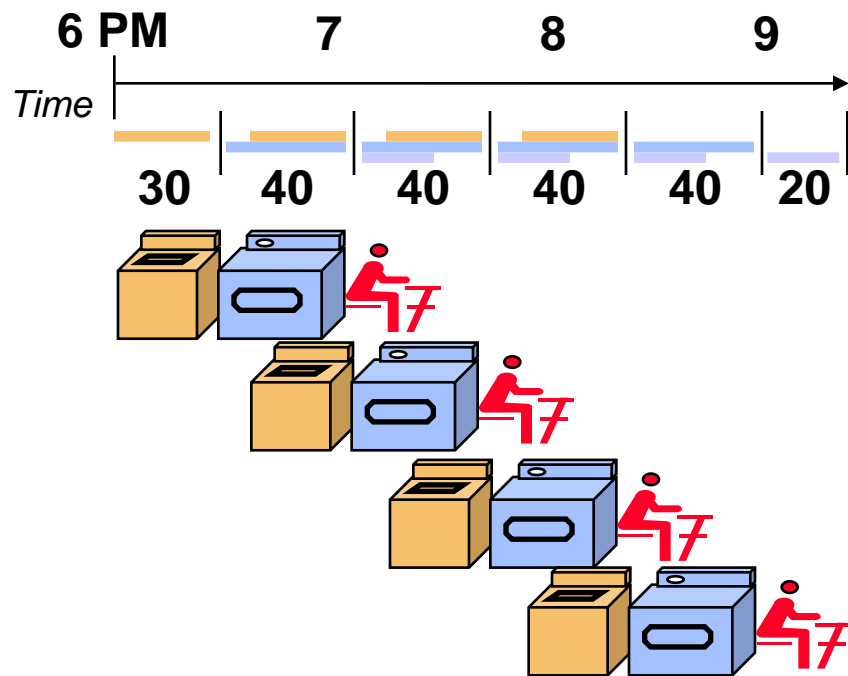

Pipelining Performance

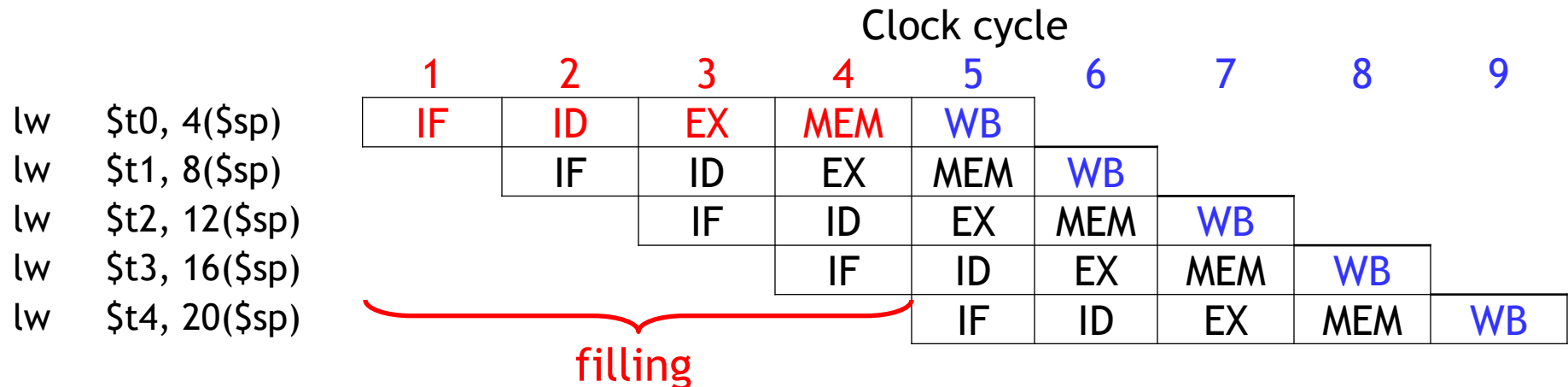

- Execution time on ideal pipeline:
 - time to fill the pipeline + one cycle per instruction
 - What is the execution time for N instructions?

- Compare with other implementations:
 - Single Cycle: (8ns clock period)

- How much faster is pipelining for N=1000 ?


Pipeline Datapath: Resource Requirements

	Clock cycle								
	1	2	3	4	5	6	7	8	9
lw \$t0, 4(\$sp)	IF	ID	EX	MEM	WB				
lw \$t1, 8(\$sp)		IF	ID	EX	MEM	WB			
lw \$t2, 12(\$sp)			IF	ID	EX	MEM	WB		
lw \$t3, 16(\$sp)				IF	ID	EX	MEM	WB	
lw \$t4, 20(\$sp)					IF	ID	EX	MEM	WB

- We need to perform several operations in the same cycle.
 - Increment the PC and add registers at the same time.
 - Fetch one instruction while another one reads or writes data.
- What does this mean for our hardware?


Pipelining other instruction types

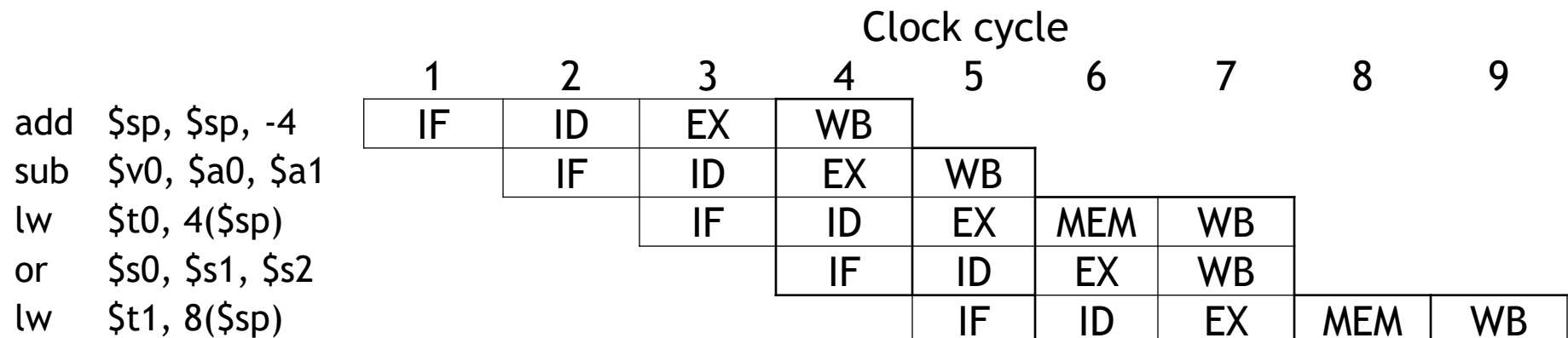- R-type instructions only require 4 stages: IF, ID, EX, and WB
 - We don't need the MEM stage
- What happens if we try to pipeline loads with R-type instructions?




Important Observation

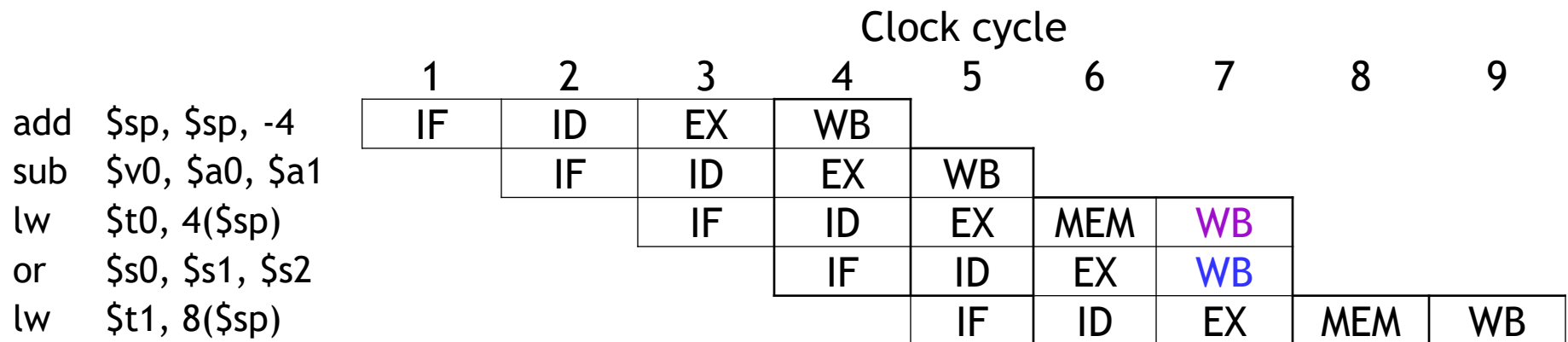- Each functional unit can only be used **once** per instruction
- Each functional unit must be used at the **same** stage for all instructions.
See the problem if:
 - Load uses Register File's Write Port during its **5th** stage
 - R-type uses Register File's Write Port during its **4th** stage



A solution: Insert NOP stages

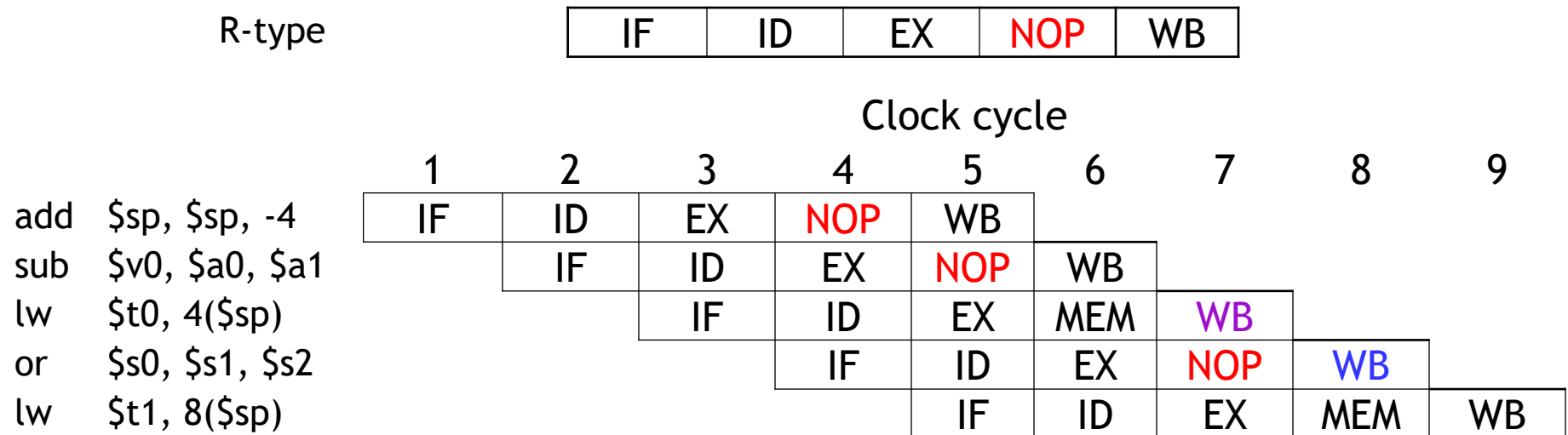- Enforce uniformity
 - Make all instructions take 5 cycles.
 - Make them have the same stages, in the same order
 - Some stages will **do nothing** for some instructions



- Stores and Branches have **NOP** stages, too...

store

IF	ID	EX	MEM	NOP
----	----	----	-----	-----

branch

IF	ID	EX	NOP	NOP
----	----	----	-----	-----

Summary

- Pipelining attempts to maximize instruction throughput by overlapping the execution of multiple instructions.
- Pipelining offers amazing speedup.
 - In the best case, one instruction finishes on every cycle, and the speedup is equal to the pipeline depth.
- The pipeline datapath is much like the single-cycle one, but with added pipeline registers
 - Each stage needs its own functional units
- Next time we'll see the datapath and control, and walk through an example execution.